

CLASS 10TH WORKSHEET CHAPTER – CURRENT ELECTRICITY

Exercise 8(A) — Multiple Choice Type

Question 1

The charge on an electron is :

1. $+1.6 \times 10^{-19} \text{ C}$
2. $-1.6 \times 10^{-20} \text{ C}$
3. $+1.6 \times 10^{20} \text{ C}$
4. $-1.6 \times 10^{-19} \text{ C}$

Answer

$-1.6 \times 10^{-19} \text{ C}$

Reason — The charge on an electron is $-1.6 \times 10^{-19} \text{ C}$.

Question 2

The number of electrons in 1 C charge is :

1. 6.25×10^{18}
2. 6.25×10^{19}
3. 6.25×10^{25}
4. 1.6×10^{-19}

Answer

6.25×10^{18}

Reason — The number of electrons in 1 C charge is 6.25×10^{18} .

Question 3

The current in a circuit is measured by by connecting it in

1. voltmeter, series
2. voltmeter, parallel
3. ammeter, series
4. ammeter, parallel

Answer

ammeter, series

Reason — By connecting the ammeter in series, the entire current flowing through the circuit also flows through the ammeter, allowing it to measure the current accurately.

Question 4

If n electrons pass through a cross-section of a conductor in time t , then current in conductor is :

1. $I = \frac{ne}{t}$
2. $I = net$
3. $I = \frac{nt}{e}$
4. $I = \frac{e}{et}$

Answer

$I = \frac{ne}{t}$

Reason — If n electrons pass through a cross-section of a conductor in time t , then current in conductor is $I = \frac{ne}{t}$

Question 5

If W joule of work is done in bringing a test charge Q coulomb from infinity to the point P , then electric potential V at point P is :

1. $V = WQ$
2. $V = Q/W$
3. $V = W/Q$
4. none of the above

Answer

$V = W/Q$

Reason — If W joule of work is done in bringing a test charge Q coulomb from infinity to the point P , then electric potential V at point P is $V = W/Q$.

Question 6

Potential at a point is said to be 1 volt, when of work is done in bringing 1 coulomb charge from infinity to that point.

1. 1 joule
2. 5 joule
3. 10 joule
4. 1 erg

Answer

1 joule

Reason — The potential at a point is defined as 1 volt when 1 joule of work is done in bringing 1 coulomb charge from infinity to that point.

Question 7

The potential difference between two points in an electric circuit is measured by a which is connected in with the circuit.

1. voltmeter, series
2. voltmeter, parallel
3. ammeter, series
4. ammeter, parallel

Answer

voltmeter, parallel

Reason — Connecting the voltmeter in parallel ensures that it measures the potential difference accurately because it doesn't affect the current flow in the circuit.

Question 8

The obstruction offered to the flow of current by a wire is called :

1. current
2. potential
3. resistance
4. charge

Answer

resistance

Reason — The obstruction offered to the flow of current by a wire is called the resistance.

Question 9

According to Ohm's law :

1. $I \propto V$
2. $V/I = \text{constant}$
3. $V = IR$
4. All of the above

Answer

All of the above

Reason — According to Ohm's Law : $V = IR$

Hence, $I \propto V$ and $V/I = \text{constant}$

Hence, all are correct.

Question 10

1 ohm is equal to:

1. 1 volt
2. Volt x ampere
3. volt/ampere
4. all of the above

Answer

volt/ampere

Reason — 1 ohm = volt/ampere

Question 11

The unit of conductance is :

1. volt
2. ohm
3. ohm^{-1}
4. ampere

Answer

ohm^{-1}

Reason — The unit of conductance is ohm^{-1} .

Question 12

Out of the following, non-ohmic resistor is :

1. nichrome
2. copper sulphate solution with copper electrodes and dil sulphuric acid.
3. solar cell
4. silver

Answer

solar cell

Reason — Nichrome, Copper sulphate solution with copper electrodes and dil sulphuric acid, Silver, all the three follow Ohm's Law i.e., $V = IR$, hence they are ohmic conductors whereas a solar cell is a non-ohmic conductor.

Question 13

The resistance of a conductor depends on :

1. the temperature of the conductor
2. the thickness of the conductor
3. the length of the conductor
4. all of the above

Answer

all of the above

Reason — The three factors on which the resistance of wire depends are —

1. **Dependence on length of the wire** — the resistance of a wire is directly proportional to the length of the wire.
 $R \propto l$
2. **Dependence on the thickness of the wire** — the resistance of a wire is inversely proportional to its area of cross section (a) normal to the direction of flow of current.
 $R \propto \frac{1}{a}$
3. **Dependence on the temperature of the wire** — the resistance of conductor increases with an increase in its temperature.

Question 14

The specific resistance of a rod of aluminium as compared to that of a thin wire of aluminium is :

1. Less
2. More
3. Same
4. Depends upon the area of cross section and length of both

Answer

Same

Reason — Specific resistance of an object is an intrinsic property which is independent of its dimensions but does depend upon nature of material and temperature. Since both rod and thin wire are of same material i.e., aluminium so both will have same specific resistance.

Question 15

If the length l of wire is increased to $3l$ by stretching, its resistance R increases to

1. $3R$
2. $4R$
3. $6R$
4. $9R$

Answer

$9R$

Reason — When the wire is stretched to thrice its length, its area of cross section becomes $1/3$ and its length becomes $3l$.

Let, a be the area of initial cross section and ρ be the specific resistance of the material of wire.

Then,

length = l ,

Resistance = $R \Omega$,

new length = $3l$,

new area = $\frac{a}{3}$

From relation

$$R = \rho \frac{l}{a} = \rho \frac{l}{\pi r^2}$$

Initial resistance $R_1 = R = \rho \frac{l}{a}$ [Equation 1]

New resistance $R_n = \rho \frac{3l}{\frac{a}{3}} = \rho \frac{9l}{a}$ [Equation 2]

On dividing eqn (ii) by (i), we get,

$$\frac{R_n}{R} = \frac{\rho \frac{9l}{a}}{\rho \frac{l}{a}} \Rightarrow \frac{R_n}{R} = 9 \Rightarrow R_n = 9R$$

Hence, the new resistance = $9R$.

Question 16

Which of the following is an ohmic resistor?

1. LED
2. junction diode
3. filament of a bulb
4. nichrome wire

Answer

nichrome wire

Reason — The conductors which obey the Ohm's law are called the ohmic resistors or linear resistances. A **Nichrome wire** obeys Ohm's law hence it is an ohmic resistor.

Question 17

For which of the following substances, resistance decreases with increase in temperature?

1. copper
2. mercury
3. carbon
4. platinum

Answer

carbon

Reason — Resistance decreases with increase in temperature for **carbon**.

Question 18

Standard resistors are made of :

1. Copper
2. Aluminium

3. Constantan
4. Carbon

Answer

Constantan

Reason — Standard resistors are made of constantan as it has high specific resistance and the effect of change in temperature on its resistance is negligible.

Question 19

The properties for which nichrome wire is used in heating appliances is/are :

1. Specific resistance is high
2. Resistance decreases with an increase in temperature
3. Resistance increases with an increase in temperature
4. Both (1) and (3)

Answer

Both (1) and (3)

Reason — Nichrome wire is commonly used in heating appliances due to its following properties:

1. Specific resistance is high — Nichrome wire has a relatively high specific resistance, which means it resists the flow of electric current efficiently, resulting in heating when current passes through it.
2. Resistance increases with an increase in temperature — This property is desirable for heating elements because it helps maintain a consistent level of heating even as the temperature rises.

Question 20

A super conductor is a substance of :

1. infinite conductance
2. infinite resistance
3. zero resistance
4. both (1) and (3)

Answer

both (1) and (3)

Reason — A superconductor exhibits both infinite conductance and zero resistance, allowing electric current to flow through it without any loss of energy due to resistance.

Exercise 8(A) — Very Short Question

Question 1

Write an expression connecting the resistance of a wire and specific resistance of its material. State the meaning of symbols used.

Answer

The expression is —

$$R = \rho \frac{l}{a}$$

where

R = resistance of wire

ρ = specific resistance of the material of wire

l = length of wire

a = area of cross section of wire

Question 2

State the order of specific resistance of (i) a metal, (ii) a semiconductor and (iii) an insulator.

Answer

The order of specific resistance is as follows:

1. The specific resistance is **very low for metals**, because it allows most of current to pass through it.
2. The specific resistance is **low for semiconductor**.
3. The specific resistance is **very high for insulators**, as the current won't pass through it.

Question 3

Name a substance of which the specific resistance remains almost unchanged by the increase in temperature.

Answer

The substance whose specific resistance remains almost unchanged with increase in temperature is **manganin**.

Question 4

Name the material used for (i) filament of an electric bulb and (ii) heating element of a room heater.

Answer

(i) The material used for the filament of an electric bulb is a **tungsten wire** because it has a high melting point.

(ii) The material used for the heating element of a room heater is **nichrome** because the specific resistance of nichrome is high and its resistance increases to a great extent with the increase in temperature.

Question 5

A substance has zero resistance below 1 K. What is such a substance called ?

Answer

A substance of zero resistance (or infinite conductance) at a very low temperature is called a **superconductor**.

Exercise 8(A) — Short Question

Question 1

Define the term current and state its S.I. unit.

Answer

Current is defined as **the rate of flow of charge**. The S.I. unit of charge is coulomb and therefore current is measured in coulomb per second which has been given the name **ampere (A)**.

Question 2

Define the term electric potential. State its S.I. unit.

Answer

The electric potential at a point is defined as the **amount of work done per unit charge in bringing a positive test charge from infinity to that point**. The S.I. unit of electric potential is **volt**.

Question 3

How is the electric potential difference between the two points defined? State its S.I. unit.

Answer

The potential difference (p.d.) between two points is equal to the work done per unit charge in moving a positive test charge from one point to the other. Its S.I. unit is **volt**. It is a **scalar** quantity.

Question 4

Explain the statement 'the potential difference between two points is 1 volt'.

Answer

The potential difference between two points is said to be 1 volt **if the work done in moving 1 coulomb charge from one point to other is 1 joule** i.e.,

$$1 \text{ volt} = \frac{1 \text{ joule}}{1 \text{ coulomb}} = 1 \text{ J C}^{-1}$$

Question 5

(a) State whether the current is a scalar or vector? What does the direction of current convey?

(b) State whether the potential is a scalar or vector? What does the positive and negative sign of potential convey?

Answer

(a) Current is a **scalar** quantity.

By stating the direction of current in a conductor we mean that the **direction of motion of electrons is opposite to it**.

(b) Potential is a **scalar** quantity.

When the **potential is positive** at a point in the vicinity of a positive charge since **work has to be done on the positive test charge against the repulsive force due to the positive charge in bringing it from infinity**, while it is **negative** at a point in the vicinity of a negative charge since the **attractive force on test charge due to the negative charge does work by itself**.

Question 6

Define the term resistance. State its S.I. unit.

Answer

The **obstruction offered to the flow of current by the conductor (or wire)** is called its resistance.

The S.I. unit of resistance is **Ohm**.

Question 7

(a) Name the particles which are responsible for the flow of current in a metallic wire.

(b) Explain the flow of current in a metallic wire on the basis of movement of the particles named by you above in part (a).

(c) What is the cause of resistance offered by the metallic wire in the flow of current through it?

Answer

(a) The particles which are responsible for the flow of current in a metallic wire are **free electrons**.

(b) In a metallic wire, the moving charges are the free electrons which constitute the current.


If n electrons pass through the cross section of a conductor in time t , then total charge passed through the conductor is given as

$$Q \text{ (charge)} = n \times e$$


and the current in conductor is

$$I = \frac{Q}{t} = \frac{ne}{t}$$

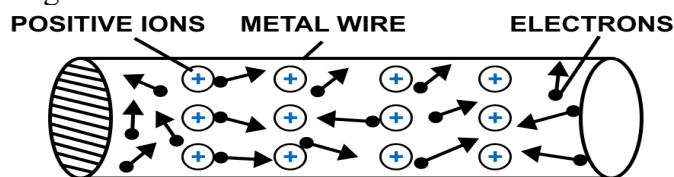(c) When the ends of a metal wire are connected to a cell, the electrons inside it experience a force in direction from the end at negative potential to positive, due to which they began to move as shown in the diagram below.



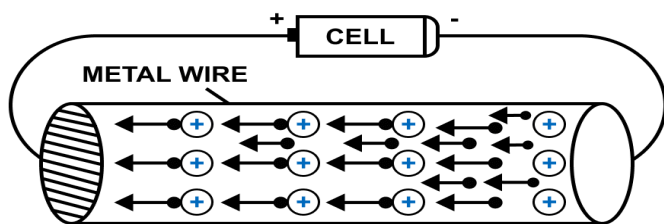(a) When no potential difference is applied



(b) When potential difference is applied

Due to force, their speed increases but during the movement they collide with the fixed positive ions and lose some of their kinetic energy due to which their speed decreases. This lost energy heats up the wire. After the collision, they are again accelerated towards the positive potential due to the existing potential difference so their speeds again increase and then again in collision with the positive ions, their speed decreases. This process continues. As a result, the electrons do not move in bulk with a continuously increasing speed, but there is a drift of electrons towards the positive terminal. Thus, a metal wire offers some resistance to the flow of electrons through it.

Question 8

(a) Name and state the law which relates the potential difference and current in a conductor.

(b) What is the necessary condition for a conductor to obey the law named above in part (a)?

Answer

(a) The law which relates the potential difference and current in a conductor is known as **Ohm's law**.

Ohm's law states that **the current flowing through the conductor is directly proportional to the potential difference across its ends provided that the physical conditions and the temperature of the conductor remain constant**.

(b) The necessary condition for a conductor to obey Ohm's law is that **the physical conditions and the temperature should remain constant.**

Question 9


Give two differences between an ohmic and non-ohmic resistor.

Answer

Ohmic resistor	Non-ohmic resistor
It obeys the Ohm's law i.e., $\frac{V}{I}$ is constant for all values of V and I.	It does not obey the Ohm's law i.e., $\frac{V}{I}$ is not same for all values of V and I.
The graph for potential difference V versus current I is a straight line passing through the origin.	The graph for potential difference V versus current I is not a straight line, but is a curve which may not pass through the origin.

Question 10

Figure below shows the I-V curves for two resistors. Identify the ohmic and non-ohmic resistors. Give a reason for your answer.

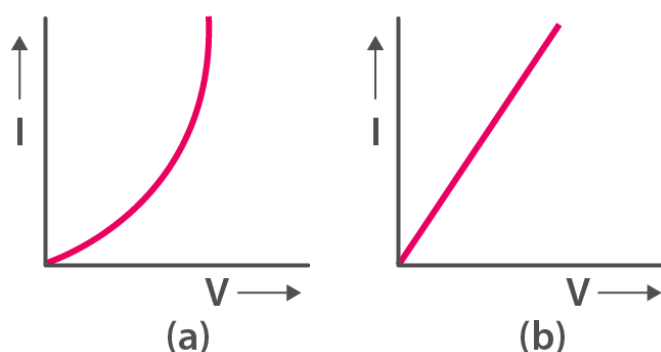

Answer

Graph (a) is **non-ohmic resistor** and

Graph (b) is **ohmic resistor**.

The I-V graph for (b) is a straight line or linear while for (a), the graph is a curve.

Question 11

How does the resistance of a wire depend on its length? Give a reason for your answer.

Answer

Resistance of a wire is directly proportional to the length of the wire.

$$R \propto l$$

In a long conductor, the number of collisions of free electrons with the positive ions will be more as compared to a shorter one. Therefore, a longer conductor offers more resistance. Hence, the resistance of a conductor is directly proportional to the length of the wire.

Question 12

How does the resistance of a metallic wire depend on its temperature? Explain with reason.

Answer

With the increase in temperature of a conductor, the random motion of electrons increases. As a result, the number of collisions of electrons with the positive ions increase. Hence, the **resistance of a conductor increases with an increase in its temperature.**

Question 13

Two wires, one of copper and other of iron, are of the same length and same radius. Which will have more resistance? Give reason.

Answer

The **iron wire** will have more resistance.

Iron wire has more resistance as compared to copper because **specific resistance of iron is more than that of copper.**

Question 14

Name three factors on which resistance of a given wire depends and state how it is affected by the factors stated by you?

Answer

The three factors on which the resistance of wire depends are —

1. **Dependence on length of the wire** — the resistance of a wire is directly proportional to the length of the wire.
 $R \propto l$
2. **Dependence on the thickness of the wire** — the resistance of a wire is inversely proportional to its area of cross section (a) normal to the direction of flow of current.
 $R \propto \frac{1}{a}$
3. **Dependence on the temperature of the wire** — the resistance of conductor increases with an increase in its temperature.

Question 15

Define the term specific resistance and state its S.I. unit.

Answer

Specific resistance of a material is the resistance of a wire of that material of unit length and unit area of cross section.

The S.I. unit of specific resistance is **ohm \times metre or (Ω m)**

Question 16

- (a) Name two factors on which the specific resistance of a wire depends?
- (b) Two wires A and B are made of copper. The wire A is long and thin while the wire B is short and thick. Which will have more specific resistance?

Answer

- (a) Two factors on which the specific resistance of a wire depends are —
1. **Material of the substance** — It is a characteristic property of the substance. It is different for different substances.
 2. **Temperature of the substance** — It increases with the increase in temperature for metals, but it decreases with the increase in temperature for the semiconductor.
- (b) Both the wires will have the **same** specific resistance because the specific resistance is a characteristic property of the material and as both the wires are of copper hence both will have same specific resistance.

Question 17

How does the specific resistance of a semi-conductor change with the increase in temperature?

Answer

The specific resistance of a semi-conductor **decreases** with the increase in temperature.

Question 18

How does (a) resistance, and (b) specific resistance of a wire depend on its (i) length, and (ii) radius?

Answer

- (a) Dependency of resistance of a wire is as follows:
1. Resistance of a wire is **directly proportional to length of the wire.**
 2. Resistance of a wire is **inversely proportional to the square of radius of the wire.**
- (b) Dependency of specific resistance of a wire is as follows:
1. Specific resistance of a wire **does not depend on length of the wire** as it is a characteristic property of the material of wire.
 2. Specific resistance of a wire **does not depend on radius of the wire** as it is a characteristic property of the material of wire.

Question 19

- (a) Name the material used for making connection wires. Give reason for your answer.

(b) Why should a connection wire be thick?

Answer

(a) **Copper or aluminium** materials are used for making connection wires because their specific resistance is very low and hence they possess least possible resistance.

Due to low (or negligible) resistance of connection wires, the current in circuit remains unaffected, and the loss of energy due to heating is prevented. Hence, they are made of materials such as copper or aluminium, whose specific resistance is very small.

(b) The connection wires are made thick so that their **resistance becomes low**.

Question 20

Name a material which is used for making the standard resistor. Give a reason.

Answer

Standard resistors are made of **manganin, constantan etc.** for which the specific resistance is high and the effect of change in temperature on their resistance is negligible.

Question 21

Name the material used for making fuse wire. Give a reason.

Answer

The material used for making fuse wire is an alloy of lead and tin because its melting point is low and its specific resistance is more than that of copper or aluminium so that the resistance of a short and thin fuse wire is more than that of the connecting wire. It permits current upto its safe limit to pass through it, but an excessive current melts it so that it blows off and the circuit is broken.

Question 22

What is a superconductor ? Give one example of it.

Answer

A superconductor is a **substance of zero resistance (or infinite conductance) at a very low temperature**.

Example — **Mercury below 4.2 K, lead below 7.25 K and niobium below 9.2 K**

Resistances of these substances decrease tremendously with the decrease in temperature and become almost zero in the low temperature range near absolute zero. Zero resistance of a superconductor means its infinite conductivity (i.e., once a current starts flowing in a superconductor, it persists even when there is no potential across it).

Exercise 8(A) — Long Questions

Question 1


State Ohm's law and draw a neat labelled circuit diagram containing a battery, a key, a voltmeter, an ammeter, a rheostat and an unknown resistance to verify it.

Answer

According to Ohm's law, **the current flowing in a conductor is directly proportional to the potential difference applied across its ends provided that the physical conditions and the temperature of the conductor remain constant**.

If a current I flows in a conductor when the potential difference across its ends is V and R is the resistance, then according to Ohm's law $V = IR$

Below circuit diagram shows the setup for verifying Ohm's law:

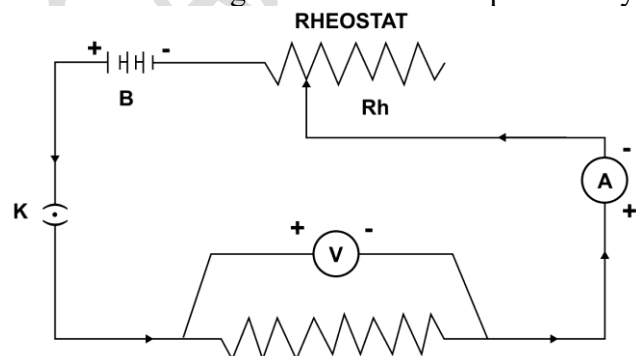


Question 2

- (a) Draw a V-I graph for a conductor obeying Ohm's law.
(b) What does the slope of V-I graph for a conductor represent?

Answer

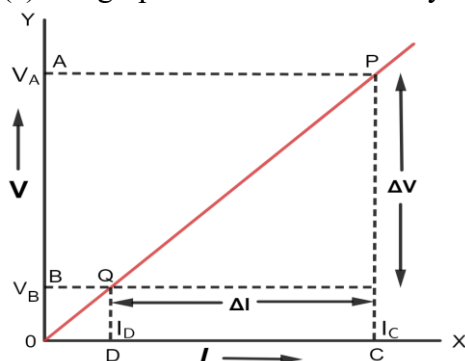- (a) V-I graph for a conductor obeying Ohm's law is shown below:




- (b) Slope of V-I graph for a conductor represents **resistance**.

Question 3

Draw an I-V graph for a linear resistor. What does its slope represent?

Answer

I-V graph for a linear resistor

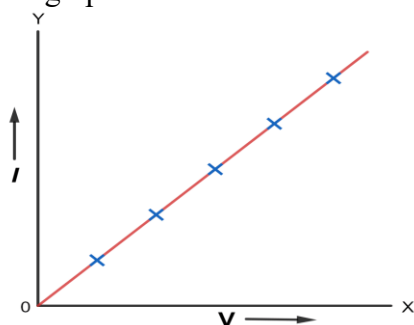

Slope of I-V graph — The slope of I-V graph is $\frac{\Delta I}{\Delta V}$ which is the reciprocal of resistance of the conductor i.e.,

$$\text{Slope} = \frac{\Delta I}{\Delta V} = \frac{1}{\text{resistance of the conductor}}$$


Question 4

What is an ohmic resistor? Give one example of an ohmic resistor. Draw a graph to show its current-voltage relationship. How is the resistance of the resistor determined from this graph?

Answer

The **conductors which obey the Ohm's law** are called the ohmic resistors or linear resistances. Examples are all metallic conductors (such as Silver, Aluminium, Copper, Iron etc.)

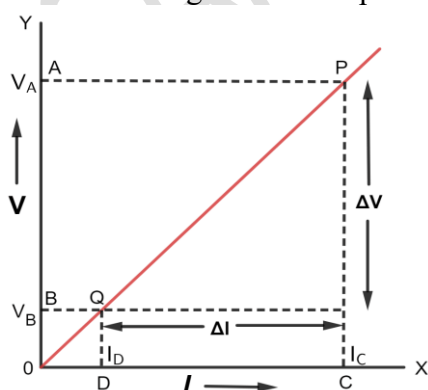Current-Voltage relationship of an ohmic resistor is shown in the below graph:



Resistance is determined in the form of **slope** from the graph.


Question 5

What are non-ohmic resistors? Give one example and draw a graph to show its current-voltage relationship.

Answer

The **conductors which do not obey the Ohm's law** are known as the non-ohmic resistors (or non-linear resistances). Examples — LED, solar cell, junction diode, etc.

Current-Voltage relationship of non-ohmic resistors is shown in the graph below:

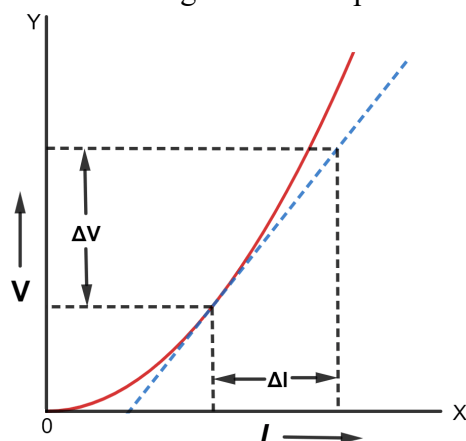

Question 6

Draw a V-I graph for a conductor at two different temperatures. What conclusion do you draw from your graph for the variation of resistance of conductor with temperature?

Answer

V-I graph of a conductor at two different temperatures T_1 and T_2 is shown below:

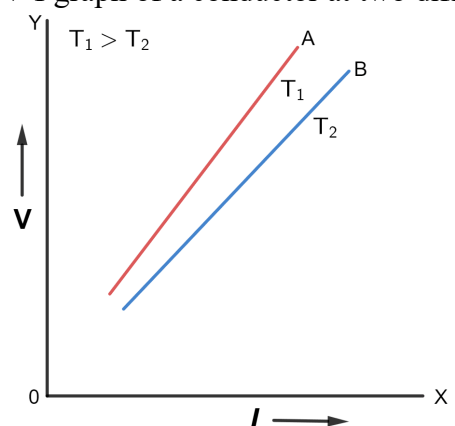


Figure shows two straight lines A and B on the V-I graph for a conductor at two different temperatures T_1 and T_2 ($T_1 > T_2$) respectively.

The straight line A is more steeper than the line B because the resistance of conductor is more at high temperature T_1 than at low temperature T_2

Question 7

(a) How does the resistance of a wire depend on its radius? Explain your answer.

(b) Two copper wires are of same length, but one is thicker than the other. Which will have more resistance?

Answer

(a) In a thick conductor, electrons get a larger area of cross section to flow as compared to a thin conductor, therefore **a thick wire offers less resistance**. The resistance of a conductor is inversely proportional to its area of cross section (a), normal to the direction of flow of current i.e.,

$$R \propto \frac{1}{a}$$

Hence,

$$R \propto \frac{1}{\pi r^2}$$

where r is the radius of the wire.

Hence, resistance of a wire is **inversely proportional to the square of the radius of the wire**.

(b) As we have seen above that the resistance of a conductor is inversely proportional to its area of cross section (a), normal to the direction of flow of current. Hence, the thin wire, will offer more resistance as its area of cross section is less.

Exercise 8(A) — Numericals

Question 1

In a conductor, 6.25×10^{16} electrons flow from its end A to B in 2 s. Find the current flowing through the conductor. ($e = 1.6 \times 10^{-19}$ C)

Answer

Given,

Number of electrons flowing (n) = 6.25×10^{16}

Time taken (t) = 2 s

$e = 1.6 \times 10^{-19}$ C

Current in conductor is given by,

$$I = \frac{ne}{t}$$

Substituting the values in the formula above we get,

$$I = \frac{6.25 \times 10^{16} \times 1.6 \times 10^{-19}}{2} \quad I = \frac{6.25 \times 1.6 \times 10^{-3}}{2} \quad I = 6.25 \times 0.8 \times 10^{-3} \quad I = 5 \times 10^{-3} \text{ A}$$

Hence, the **current flowing through the conductor = 5 mA from B to A**

Question 2

A current of 3.2 mA flows through a conductor. If charge on an electron is -1.6×10^{-19} coulomb, find the number of electrons that will pass each second through the cross section of that conductor.

Answer

Given,

Current (I) = 3.2 mA = 3.2×10^{-3} A

Charge of one electron = -1.6×10^{-19} coulomb

$t = 1$ s

Charge flowing through the conductor in one second

Charge (Q) = current (I) \times time (t)

Substituting the values in the formula above we get,

$$Q = 3.2 \times 10^{-3} \times 1 = 3.2 \times 10^{-3}$$

Hence,

$$\begin{aligned} \text{No. of electrons} &= \frac{\text{Total charge flowing}}{\text{Charge on one electron}} \\ &= \frac{3.2 \times 10^{-3}}{1.6 \times 10^{-19}} = 2 \times 10^{16} \end{aligned}$$

Therefore, **the number of electrons that will pass each second through the cross section of that conductor = 2×10^{16}**

Question 3

Find the potential difference required to flow a current of 300 mA in a wire of resistance 20 Ω .

Answer

Given,

Current (I) = 300 mA = 0.3 A

Resistance (R) = 20 Ω

Potential difference (V) = ?

From Ohm's law

$$V = IR$$

Substituting the values in the formula above, we get,

$$V = 0.3 \times 20$$

$$V = 6 \text{ V}$$

Hence, the required potential difference = 6 V

Question 4

An electric bulb draws 1.2 A current at 6.0 V. Find the resistance of filament of bulb while glowing.

Answer

Given,

$$\text{Current (I)} = 1.2 \text{ A}$$

$$\text{Potential difference (V)} = 6.0 \text{ V}$$

$$\text{Resistance (R)} = ?$$

From Ohm's law

$$V = IR$$

Substituting the values in the formula above, we get,

$$6 = 1.2 \times R$$

$$\Rightarrow R = \frac{6}{1.2}$$

$$\Rightarrow R = 5 \Omega$$

Hence, resistance of filament of bulb = 5 Ω

Question 5

A car bulb connected to a 12 volt battery draws 2 A current when glowing. What is the resistance of the filament of the bulb? Will the resistance be more, same or less when the bulb is not glowing.

Answer

Given,

$$\text{Potential difference (V)} = 12 \text{ V}$$

$$\text{Current (I)} = 2 \text{ A}$$

$$\text{Resistance} = ?$$

From Ohm's law

$$V = IR$$

Substituting the values in the formula above, we get,

$$12 = 2 \times R$$

$$\Rightarrow R = \frac{12}{2}$$

$$\Rightarrow R = 6 \Omega$$

Hence, the resistance of the filament of the bulb = 6 Ω

The resistance will be less when the bulb is not glowing.

Question 6

Calculate the current flowing through a wire of resistance 5 Ω connected to a battery of potential difference 3 V.

Answer

Given,

$$\text{Resistance (R)} = 5 \text{ Ohm}$$

$$\text{Potential difference (V)} = 3 \text{ V}$$

$$\text{Current (I)} = ?$$

From Ohm's law

$$V = IR$$

Substituting the values in the formula above, we get,

$$3 = I \times 5$$

$$\Rightarrow I = \frac{3}{5}$$

$$\Rightarrow I = 0.6 \text{ A}$$

Hence, the current flowing through the wire = 0.6 A

Question 7

In an experiment of verification of Ohm's law, following observations are obtained.


Potential difference V (in volt)	0.5	1.0	1.5	2.0	2.5
Current I (in amp)	0.2	0.4	0.6	0.8	1.0

Draw a V-I graph and use this graph to find —

- the potential difference V when the current I is 0.5 A.
- the current I when the potential difference V is 0.75 V.
- the resistance in circuit.

Answer

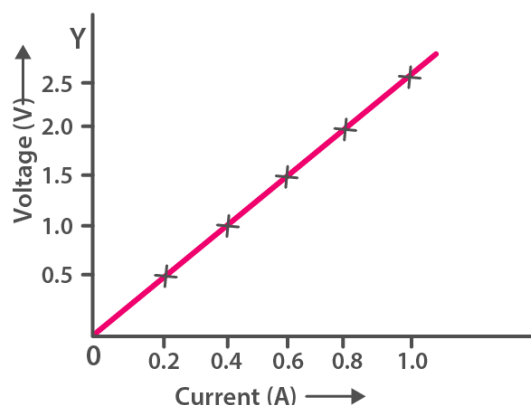V-I graph for the readings is shown below:



- We can observe from the graph that when current is 0.5 A then potential difference is **1.25 V**.
- We can observe from the graph that when potential difference is 0.75 V, then current is **0.3 A**.
- Slope of the graph gives the resistance, and as the graph is linear

So, if potential difference (V) = 1.0 V

current (I) = 0.4 A

From Ohm's law

$$V = IR$$

Substituting the values in the formula above, we get,

$$1.0 = 0.4 \times R$$

$$\Rightarrow R = \frac{1.0}{0.4}$$

$$\Rightarrow R = \frac{10}{4}$$

$$\Rightarrow R = 2.5 \Omega$$

Hence, the resistance in circuit = **2.5 Ω**

Question 8

Two wires of the same material and same length have radii 1 mm and 2 mm respectively. Compare (i) their resistances (ii) their specific resistance.

Answer

$$(i) R = \rho \frac{l}{a} = \rho \frac{l}{\pi r^2}$$

Resistance for wire of radius 1 mm,

$$R_1 = \rho \frac{l}{\pi 1^2} = \rho \frac{l}{\pi}$$

Resistance for wire of radius 2 mm,

$$R_2 = \rho \frac{l}{\pi 2^2} = \rho \frac{l}{\pi 4}$$

Hence, ratio between the two,

$$R_1 : R_2$$

$$= \frac{\rho \frac{l}{\pi}}{\rho \frac{l}{\pi 4}} = \frac{4}{1} = 4:1$$

Hence, **the ratio of resistance between the two wires = 4 : 1**

(ii) The specific resistance of the two wires will be **same** because the specific resistance is a characteristic property of the material, hence it does not change with radius.

Therefore, ratio of specific resistance between the two wires = **1 : 1**

Question 9

A given wire of resistance $1\ \Omega$ is stretched to double its length. What will be its new resistance?

Answer

When the wire is stretched to double its length, its area of cross section becomes half and its length becomes double.

Let, a be the area of initial cross section and ρ be the specific resistance of the material of wire.

Then,

length = l ,

$R = 1\ \Omega$,

new length = $2l$,

new area = $\frac{a}{2}$

From relation

$$R = \rho \frac{l}{a} = \rho \frac{l}{\pi r^2}$$

$$\text{Initial resistance } R_1 = 1 = \rho \frac{l}{a} \quad [\text{Equation 1}]$$

$$\text{New resistance } R_n = \rho \frac{2l}{\frac{a}{2}} = \rho \frac{4l}{a} \quad [\text{Equation 2}]$$

On dividing eqn (ii) by (i), we get,

$$\frac{R_n}{1} = \frac{\rho \frac{4l}{a}}{\rho \frac{l}{a}} \Rightarrow R_n = 4\Omega$$

Hence, **the new resistance = $4\ \Omega$.**

Question 10

A wire of resistance 3 ohm and length 10 cm is stretched to length 30 cm. Assuming that it has a uniform cross-section, what will be its new resistance?

Answer

Given,

Resistance (R) = $3\ \Omega$

Length (l) = 10 cm

Let, a be the area of initial cross section and ρ be the specific resistance of the material of wire.

Then,

$R = 3\ \Omega$

length = 10 cm,

new length = 30 cm,

new area $a = \frac{a}{3}$

From relation

$$R = \rho \frac{l}{a} = \rho \frac{l}{\pi r^2}$$

$$\text{Initial resistance } 3 = \rho \frac{10}{a} \quad [\text{Equation 1}]$$

$$\text{New resistance } R_2 = \rho \frac{30}{\frac{a}{3}} = \rho \frac{90}{a} \quad [\text{Equation 2}]$$

On dividing eqn (i) by (ii), we get,

$$\frac{3}{R_2} = \frac{\rho \frac{10}{a}}{\rho \frac{90}{a}} \Rightarrow \frac{3}{R_2} = \frac{10}{90} \Rightarrow R_2 = 3 \times 9 \Rightarrow R_2 = 27\Omega$$

Hence, the new resistance = 27Ω .

Question 11

A wire of resistance 9 ohm having length 30 cm is tripled on itself. What is its new resistance?

Answer

Given,

Resistance (R) = 9Ω

When the wire is tripled on itself, its area of cross section becomes thrice and its length becomes $\frac{l}{3}$.

Let, a be the area of initial cross section and ρ be the specific resistance of the material of wire.

Then,

length = 30 cm,

new length = $\frac{l}{3} = \frac{30}{3} = 10$ cm,

new area $a_n = 3a$

From relation

$$R = \rho \frac{l}{a}$$

Initial resistance $9 = \rho \frac{30}{a}$ [Equation 1]

New resistance $R_n = \rho \frac{10}{3a}$ [Equation 2]

On dividing eqn (ii) by (i), we get,

$$\frac{R_n}{9} = \frac{\rho \frac{10}{3a} R_n}{\rho \frac{30}{a} 9} = \frac{10 R_n}{90 \cdot 9} = \frac{1}{9} R_n = 1 \Omega$$

Hence, the new resistance = 1Ω .

Question 12

What length of copper wire of specific resistance $1.7 \times 10^{-8} \Omega \text{ m}$ and radius 1 mm is required so that its resistance is 2Ω .

Answer

Given,

Specific resistance $\rho = 1.7 \times 10^{-8} \Omega \text{ m}$

Radius $r = 1 \text{ mm} = 10^{-3} \text{ m}$

Resistance $R = 2 \Omega$

Length $l = ?$

From relation

$$R = \rho \frac{l}{a} = \rho \frac{l}{\pi r^2}$$

Substituting the values in the formula above we get,

$$2 = 1.7 \times 10^{-8} \frac{l}{\pi (10^{-3})^2} \Rightarrow l = \frac{2 \times \pi (10^{-3})^2}{1.7 \times 10^{-8}} = \frac{2 \times 3.14 \times 10^{-6}}{1.7 \times 10^{-8}} = \frac{6.28 \times 10^{-6}}{1.7 \times 10^{-8}} = \frac{6.28 \times 10^{-6} \times 10^8}{1.7} = \frac{628}{1.7} \Rightarrow l = 369.4 \text{ m}$$

Hence, the length of the copper wire = 369.4 m .

Question 13

The filament of a bulb takes a current 100 mA when potential difference across it is 0.2 V. When the potential difference across it becomes 1.0 V, the current becomes 400 mA. Calculate the resistance of filament in each case and account for the difference.

Answer

Case 1 —

Current (I) = 100 mA = 0.1 A

Potential Difference (V) = 0.2 V

From Ohm's law

$$V = IR$$

Substituting the values in the formula above, we get,

$$0.2 = 0.1 \times R$$

$$\Rightarrow R = \frac{0.2}{0.1}$$

$$\Rightarrow R = 2 \Omega$$

Hence, **resistance of filament of bulb = 2Ω**

Case 2 —

$$\text{Current (I)} = 400 \text{ mA} = 0.4 \text{ A}$$

$$\text{Potential Difference (V)} = 1.0 \text{ V}$$

From Ohm's law

$$V = IR$$

Substituting the values in the formula above, we get,

$$1.0 = 0.4 \times R$$

$$\Rightarrow R = \frac{1.0}{0.4}$$

$$\Rightarrow R = 2.5 \Omega$$

Hence, **resistance of filament of bulb = 2.5Ω**

Therefore, we observe that with increase in temperature resistance of the wire increases.

Hence, **resistance of filament increases with the increase in temperature.**

Exercise 8(B) — Multiple Choice Type

Question 1

The emf of a cell depends on :

1. the material of electrodes
2. the shape of electrodes
3. the distance between the electrodes
4. the amount of electrolyte in the cell

Answer

the material of electrodes

Reason — The emf of a cell depends on :

1. the material of electrodes and
2. the electrolyte used in the cell.

Question 2

Emf of a cell is the terminal voltage when cell is not in use, while the terminal voltage when cell is in use.

1. greater than, smaller than
2. smaller than, greater than
3. equal to, greater than
4. equal to, smaller than

Answer

equal to, greater than

Reason — Emf of a cell is equal to the terminal voltage when cell is not in use and when the current starts to flow in the circuit, then there is a voltage drop due to internal resistance, thus we get, $V = E - Ir$. Hence, Emf is greater than the terminal voltage when cell is in use.

Question 3

Current drawn from the cell :

1. $I = \epsilon[R+r]$
2. $I = \frac{\epsilon}{(R+r)}$
3. $I = \epsilon R$
4. $I = \frac{E}{(r)}$

Answer

$$I = \frac{\varepsilon}{(R+r)}$$

Reason — The current drawn from the cell

$$I = \frac{\text{e.m.f. of cell}}{\text{total resistance}} = \frac{\varepsilon}{(R+r)}$$

Question 4

In series combination of resistances —

1. p.d. is same across each resistance
2. total resistance is reduced
3. current is same in each resistance
4. all of the above are true

Answer

current is same in each resistance

Reason — Current is same in each resistance in series combination of resistances. The current has a single path to flow, hence, same current passes through each resistor.

Question 5

In parallel combination of resistances :

1. p.d. is the same across each resistance
2. current is the same in each resistance
3. total resistance is increased
4. all of the above are true

Answer

p.d. is the same across each resistance

Reason — Potential difference is same across each resistor in parallel combination of resistances, which is equal to the potential difference across the terminals of the battery (or source).

Question 6

For parallel combination of resistances, which of the statements are correct ?

1. On I-V graph, the slope of line is more.
2. The potential difference across each resistance is same.
3. The current in a resistor is inversely proportional to the resistance.
4. All of the above

Answer

All of the above

Reason — For parallel combination of resistances :

1. On I-V graph, the slope of line is more because resistance in parallel combination is less than series combination.
2. The potential difference across each resistance is same because, the ends of each resistor are connected to the ends of the same source of potential.
3. According to Ohm's Law $V = IR$. Hence, the current in a resistor is inversely proportional to the resistance.

Question 7

Assertion (A): The terminal voltage of a cell is always less than its e.m.f.

Reason (R): More the current drawn from the cell, the less is the terminal voltage.

1. Both A and R are true and R is the correct explanation of A
2. Both A and R are true and R is not the correct explanation of A
3. assertion is false but reason is true.
4. assertion is true but reason is false.

Answer

assertion is false but reason is true..

Explanation

Assertion (A) is false. E.m.f. is greater than the terminal voltage only when the cell delivers the current to the external circuit.

Reason (R) is true. When a heavy current is drawn from the cell, a large number of charge carriers flow through the electrolyte and hence more work is done. This results in more voltage drop v , and hence less terminal voltage V . Thus, terminal voltage V of a cell depends on the amount of current I drawn from it.

Exercise 8(B) — Very Short Questions

Question 1

Write the expressions for the equivalent resistance R of three resistors R_1 , R_2 and R_3 joined in (a) parallel, (b) series.

Answer

(a) Equivalent resistance R of three resistors R_1 , R_2 and R_3 joined in parallel is given by —

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

(b) Equivalent resistance R of three resistors R_1 , R_2 and R_3 joined in series is given by —

$$R = R_1 + R_2 + R_3$$

Question 2

State how are the two resistors joined with a battery in each of the following cases when —


- (a) same current flows in each resistor,
- (b) potential difference is same across each resistor,
- (c) equivalent resistance is less than either of the two resistances,
- (d) equivalent resistance is more than either of the two resistances.

Answer

- (a) When same current flows in each resistor, then the two resistors are joined **in series**
- (b) When potential difference is same across each resistor, then the two resistors are joined **in parallel**
- (c) When equivalent resistance is less than either of the two resistances, then the two resistors are joined **in parallel**
- (d) When equivalent resistance is more than either of the two resistances, then the two resistors are joined **in series**

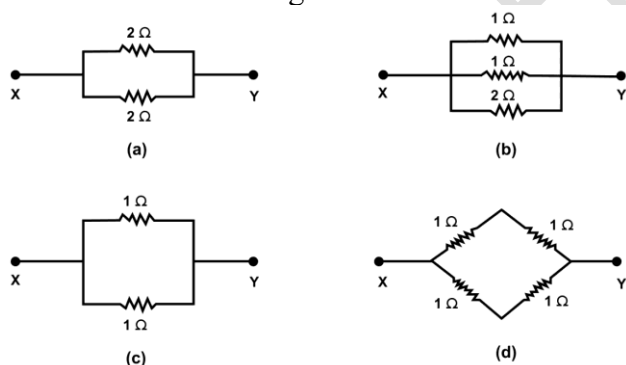Question 3

Which of the following combinations have the same equivalent resistance between X and Y?



Answer

(a) In the circuit, two resistors of 2Ω each are connected in parallel. In parallel, the equivalent resistance is R_p , then

$$\frac{1}{R_p} = \frac{1}{2} + \frac{1}{2} \Rightarrow \frac{1}{R_p} = \frac{2}{2} \Rightarrow R_p = 1\Omega$$

Hence, $R_p = 1\Omega$

(b) In the circuit, three resistors of 1Ω , 1Ω and 2Ω are connected in parallel. In parallel, the equivalent resistance is R_p , then

$$\frac{1}{R_p} = \frac{1}{1} + \frac{1}{1} + \frac{1}{2} \Rightarrow \frac{1}{R_p} = \frac{2+2+1}{2} \Rightarrow R_p = \frac{2}{5}\Omega \Rightarrow R_p = 0.4\Omega$$

Hence, $R_p = 0.4\Omega$

(c) In the circuit two resistors of $1\ \Omega$ each are connected in parallel. In parallel, the equivalent resistance is R_p , then

$$\frac{1}{R_p} = \frac{1}{1} + \frac{1}{1} = \frac{1+1}{1} = \frac{2}{1} \Rightarrow R_p = 0.5\Omega$$

Hence, $R_p = 0.5\ \Omega$

(d) In the circuit there are three parts. In the first part two resistor of $1\ \Omega$ each are connected in series. In series, the equivalent resistance is R'_s , then

$$R'_s = (1 + 1)\ \Omega = 2\ \Omega$$

In the second part two resistor of $1\ \Omega$ each are connected in series. In series, the equivalent resistance is R''_s , then

$$R''_s = (1 + 1)\ \Omega = 2\ \Omega$$

In the third part, R'_s and R''_s are in parallel, the equivalent resistance is R_p , then

$$\frac{1}{R_p} = \frac{1}{2} + \frac{1}{2} = \frac{1+1}{2} = \frac{2}{2} \Rightarrow R_p = 1\Omega$$

Hence, $R_p = 1\ \Omega$

Therefore, on observing the values we can say that (a) and (d) have same equivalent resistances i.e., $1\ \Omega$.

Exercise 8(B) — Short Questions

Question 1

State two differences between the e.m.f. and terminal voltage of a cell.

Answer

E.m.f of cell	Terminal voltage of cell
It is measured by the amount of work done per unit change in moving a positive test charge in the complete circuit inside and outside the cell.	It is measured by the amount of work done per unit charge in moving a positive test charge in the circuit outside the cell.
It is the characteristic of the cell, i.e., it does not depend on the amount of current drawn from the cell.	It depends on the amount of current drawn from the cell. More the current drawn from the cell, less is the terminal voltage.

Question 2

Name two factors on which the internal resistance of a cell depends and state how does it depend on the factors stated by you.

Answer

The factors on which the internal resistance of a cell depends are —

1. The **surface area of the electrodes** — larger the surface area of electrodes, less is the internal resistance.
2. The **distance between the electrodes** — more the distance between the electrodes, greater is the internal resistance.

Question 3

A cell of e.m.f. ϵ and internal resistance r is used to send current to an external resistance R . Write expressions for (a) the total resistance of circuit, (b) the current drawn from the cell, (c) the p.d. across the cell, and (d) voltage drop inside the cell.

Answer

Given,

e.m.f. = ϵ

internal resistance = r

external resistance = R

(a) The total resistance of circuit = $R + r$

(b) The current drawn from the cell

$$I = \frac{\text{e.m.f. of cell}}{\text{total resistance}} = \frac{\epsilon}{(R+r)}$$

(c) the p.d. across the cell = $V = IR$

Substituting from above,

$$V = \frac{\epsilon}{(R+r)} \times R$$

(d) voltage drop inside the cell $V = Ir$

Substituting from above,

$$V = \frac{\epsilon}{(R+r)} \times r$$

Question 4

A cell is used to send current to an external circuit. (a) How does the voltage across its terminals compare with its e.m.f. ? (b) Under what condition is the e.m.f. of the cell equal to its terminal voltage?

Answer


(a) When a cell is used to send current to an external circuit, its terminal voltage V is less than its e.m.f.

Hence, **terminal voltage < e.m.f.**

(b) The emf of the cell is equal to its terminal voltage when **no current is drawn**.

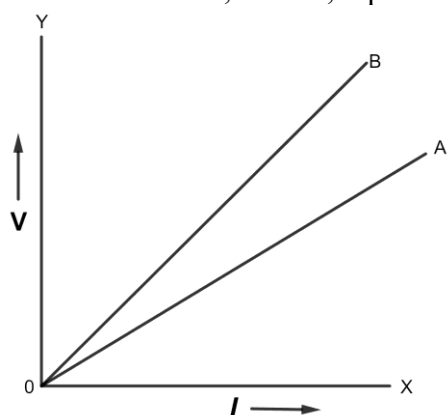Question 5

The V-I graph for a series combination and for a parallel combination of two resistors is shown in figure. Which of the two, A or B, represents the parallel combination? Give a reason for your answer.



Answer

The slope of V-I graph gives the resistance. Since the straight line A is less steeper than B, so the straight line A represents small resistance. In parallel combination, the equivalent resistance is less than in series combination so A represents the parallel combination.

Exercise 8(B) — Long Questions

Question 1

Explain the meaning of the terms e.m.f., terminal voltage and internal resistance of a cell.

Answer

e.m.f — e.m.f of a cell is defined as the energy spent (or the work done) per unit charge in taking a positive test charge around the complete circuit of the cell. (i.e., in the circuit outside the cell as well as in the electrolyte inside the cell).

Terminal voltage — The terminal voltage of a cell is defined as the work done per unit charge in carrying a positive test charge around the circuit connected across the terminals of the cell.

Internal resistance — The resistance offered by the electrolyte inside the cell, to the flow of current, is known as the internal resistance of the cell.

Question 2

Explain why is the p.d. across the terminals of a cell is more in an open circuit and reduced in a closed circuit.

Answer

In a closed circuit, the current flows through the circuit. There is a fall of potential across the internal resistance of the cell. Hence, the p.d. across the terminals in a closed circuit is less than the p.d. across the terminals in an open circuit by an amount equal to the potential drop across the internal resistance of the cell.


Hence, the p.d. across the terminals of a cell is more in an open circuit and reduced in a closed circuit.

Question 3

How would you connect two resistors in series? Draw a diagram. Calculate the total equivalent resistance.

Answer

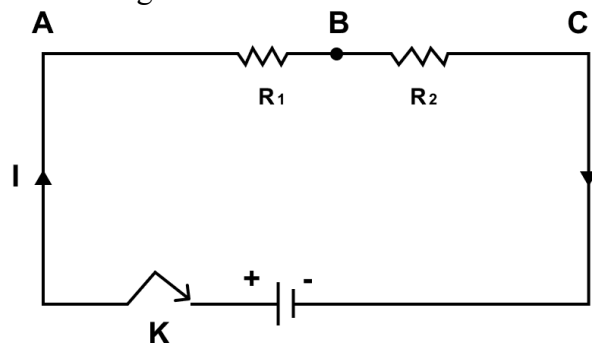Below diagram shows two resistors connected in series:



If current I is drawn from the battery, the current through each resistor will also be I .

By Ohm's law,

$$\text{p.d. between A and B is } V_1 = V_A - V_B = IR_1$$

$$\text{p.d. between B and C is } V_2 = V_B - V_C = IR_2$$

Adding these we get,

$$V = V_1 + V_2$$

$$= V_A - V_B + V_B - V_C$$

$$= V_A - V_C$$

$$= IR_1 + IR_2$$

$$= I(R_1 + R_2) \quad [\text{Equation 1}]$$

If the equivalent resistance between the points A and C is R_S , then the potential difference between the points A and C is

$$V = V_A - V_C = IR_S \quad [\text{Equation 2}]$$

Therefore from equation 1 and 2,

$$IR_S = I(R_1 + R_2)$$

$$\Rightarrow R_S = R_1 + R_2$$


Thus, in the series combination, the equivalent resistance is equal to the sum of the individual resistances.

Question 4

Show by a diagram how two resistors R_1 and R_2 are joined in parallel. Obtain an expression for the total resistance of combination.

Answer

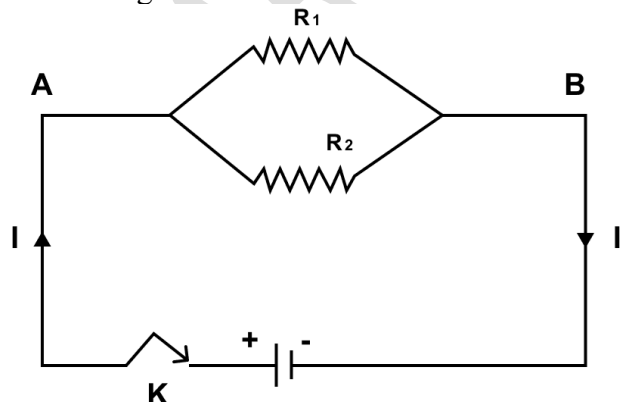Below diagram shows two resistors connected in parallel:



Let I_1 and I_2 be the currents through the resistances R_1 and R_2 respectively, then total current drawn from the battery is

$$I = I_1 + I_2 \quad [\text{Equation 1}]$$

If potential difference between the two ends A and B is V, then by Ohm's law

$$\text{current in } R_1 \text{ is } I_1 = \frac{V}{R_1}$$

$$\text{current in } R_2 \text{ is } I_2 = \frac{V}{R_2}$$

On adding these,

$$I_1 + I_2 = \frac{V}{R_1} + \frac{V}{R_2} \quad [\text{Equation 2}]$$

If the equivalent resistance of the combination between the points A and C is R_p , then total current drawn from the source is

$$I = \frac{V}{R_p} \quad [\text{Equation 3}]$$

Substituting the values of I and $I_1 + I_2$ from equation 3 and 2 in 1, we get,


$$\frac{V}{R_p} = V \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \Rightarrow \frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

Thus, in the parallel combination, the reciprocal of the equivalent resistance is equal to the sum of the reciprocals of the individual resistances.

Exercise 8(B) — Numericals

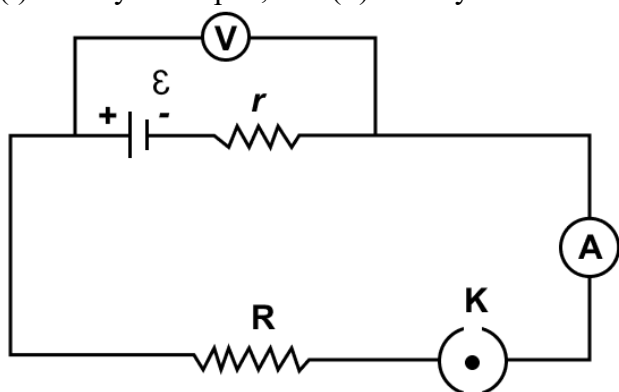Question 1

The diagram in figure shows a cell of e.m.f. $\varepsilon = 4$ volt and internal resistance $r = 2$ ohm connected to an external resistance $R = 8$ ohm. The ammeter A measures the current in the circuit and the voltmeter V measures the terminal voltage across the cell. What will be the readings of the ammeter and voltmeter when (i) the key K is open, and (ii) the key K is closed.



Answer

Given,

e.m.f. $\varepsilon = 4$ volt

resistance $r = 2$ ohm

external resistance $R = 8$ ohm

(i) When the key is open then no current is flowing in the circuit and hence the **ammeter reading = 0**

From relation,

$$\text{Voltage (V)} = \varepsilon - Ir$$

Substituting the values in the formula we get,

$$V = 4 - (0 \times 2)$$

$$V = 4 \text{ volt}$$

Hence, **voltmeter reading = 4 volt**

(ii) When key is closed, current drawn from the cell,

$$I = \frac{\text{e.m.f. of cell}}{\text{total resistance}} = \frac{\varepsilon}{R + r}$$

Substituting the values in the formula above we get,

$$I = \frac{4}{8+2}$$

$$\Rightarrow I = \frac{4}{10}$$

$$\Rightarrow I = 0.4 \text{ ampere}$$

Hence, **ammeter reading = 0.4 ampere**

From relation,

$$\text{Voltage (V)} = \varepsilon - Ir$$

Substituting the values in the formula we get,

$$V = 4 - (0.4 \times 2) = 3.2 \text{ V}$$

Hence, **voltmeter reading = 3.2 volt**

Question 2

A battery of e.m.f. 6.0 V supplies current through a circuit in which resistance can be changed. A high resistance voltmeter is connected across the battery. When the current is 3 A, the voltmeter reads 5.4 V. Find the internal resistance of the battery.

Answer

Given,

$$\text{e.m.f. } (\varepsilon) = 6.0 \text{ V}$$

$$\text{Current (I)} = 3 \text{ A}$$

$$\text{Potential difference (V)} = 5.4 \text{ V}$$

$$r = ?$$

From relation,

$$V = \varepsilon - Ir$$

Substituting the values in the formula above we get,

$$5.4 = 6 - (3r)$$

$$\Rightarrow r = 6 - 5.4$$

$$\Rightarrow 3r = 0.6$$

$$\Rightarrow r = \frac{0.6}{3}$$

$$\Rightarrow r = \frac{6}{30}$$


$$\Rightarrow r = \frac{2}{10}$$

$$\Rightarrow r = 0.2 \Omega$$

Hence, **internal resistance of the battery = 0.2 Ω**

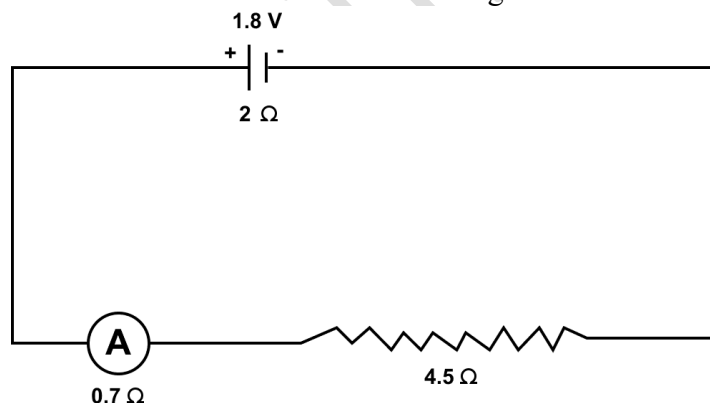Question 3

A cell of emf 1.8 V and internal resistance 2 Ω is connected in series with an ammeter of resistance 0.7 Ω and resistance of 4.5 Ω as shown in figure.



(a) What would be the reading of the ammeter?

(b) What is the potential difference across the terminals of the cell ?

Answer

(a) Given,

$$\text{e.m.f. } (\varepsilon) = 1.8 \text{ V}$$

$$\text{Internal resistance (r)} = 2 \Omega$$

$I = ?$

Total resistance of arrangement = $2 + 0.7 + 4.5 = 7.2 \Omega$

From relation,

$$I = \frac{\varepsilon}{R}$$

Substituting the values in the formula above we get,

$$I = \frac{1.8}{7.2}$$

$$\Rightarrow I = 0.25 \text{ A}$$

Hence, **reading of ammeter = 0.25 A**

(b) Current (I) = 0.25 A

total resistance (excluding internal resistance) = $4.5 + 0.7 = 5.2 \text{ ohm}$

Using ohm's law

$$V = IR$$

Substituting the values in the formula above we get,

$$V = 0.25 \times 5.2$$

$$V = 1.3 \text{ V}$$

Hence, **potential difference across the terminals of the battery = 1.3 V**

Question 4

A music system draws a current of 400 mA when connected to a 12 V battery.

(a) What is the resistance of the music system ?

(b) The music system if left playing for several hours and finally the battery voltage drops and the music system stops playing when the current drops to 320 mA. At what battery voltage does the music system stop playing.

Answer

(a) Given,

$$I = 400 \text{ mA} = 400 \times 10^{-3} = 0.4 \text{ A}$$

$$V = 12 \text{ V}$$

From Ohm's law,

$$V = IR$$

Substituting the values in the formula we get,

$$12 = 0.4 \times R$$

$$\Rightarrow R = \frac{12}{0.4}$$

$$\Rightarrow R = 30 \Omega$$

Hence, **the resistance of the music system = 30 Ω**

(b) Given,

$$I = 320 \text{ mA} = 320 \times 10^{-3} \text{ A} = 0.32 \text{ A}$$

$$R = 30 \Omega$$

From Ohm's law,

$$V = IR$$

Substituting the values in the formula we get,

$$V = 0.32 \times 30 = 9.6 \text{ V}$$

Hence, **the battery voltage when the music system stops playing = 9.6 V**

Question 5

A cell of e.m.f. ε and internal resistance r sends a current of 1.0 A when it is connected to an external resistance of 1.9 ohm. But it sends a current of 0.5 A when it is connected to an external resistance of 3.9 ohm. Calculate the values of ε and r .

Answer

Given,

$$\text{e.m.f.} = \varepsilon$$

$$\text{internal resistance} = r$$

current (I) = 1.0 A

external resistance (R) = 1.9 ohm

Case 1

From relation,

$$\varepsilon = I(R + r)$$

Substituting the value in the formula above we get,

$$\varepsilon = 1(1.9 + r)$$

$$\varepsilon = 1.9 + r \quad [\text{Equation 1}]$$

In second case,

$$I = 0.5 \text{ A,}$$

$$R = 3.9 \Omega$$

Substituting the value in the formula above we get,

$$\varepsilon = 0.5(3.9 + r)$$

$$\varepsilon = 1.95 + 0.5r \quad [\text{Equation 2}]$$

Equating 1 and 2 we get,

$$1.9 + r = 1.95 + 0.5r \quad r - 0.5r = 1.95 - 1.9 \quad 0.5r = 0.05 \Rightarrow r = \frac{0.05}{0.5} \Rightarrow r = 0.1 \Omega$$

Now, substituting the value of r in equation 1, we get,

$$\varepsilon = 1.9 + 0.1$$

$$\varepsilon = 2 \text{ V}$$

Hence, $\varepsilon = 2 \text{ V}$, $r = 0.1 \Omega$

Question 6

Two resistors having resistance 8Ω and 12Ω are connected in parallel. Find their equivalent resistance.

Answer

In parallel, if the equivalent resistance is R_p , then

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} \quad \frac{1}{R_p} = \frac{1}{8} + \frac{1}{12} \quad \frac{1}{R_p} = \frac{3 + 2}{24} \quad \frac{1}{R_p} = \frac{5}{24} \Rightarrow R_p = \frac{24}{5} \Rightarrow R_p = 4.8 \Omega$$

Hence, **equivalent resistance = 4.8Ω**

Question 7

Four resistors each of resistance 5Ω are connected in parallel. What is the effective resistance?

Answer

Give,

$$R_1 = R_2 = R_3 = R_4 = 5 \Omega$$

In parallel, if the equivalent resistance is R_p , then

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \quad \frac{1}{R_p} = \frac{1}{5} + \frac{1}{5} + \frac{1}{5} + \frac{1}{5} \quad \frac{1}{R_p} = \frac{4}{5} \Rightarrow R_p = \frac{5}{4} \Rightarrow R_p = 1.25 \Omega$$


Hence, **equivalent resistance = 1.25Ω**

Question 8

You have three resistors of values 2Ω , 3Ω and 5Ω . How will you join them so that the total resistance is less than 1Ω ? Draw diagram and find the total resistance.

Answer

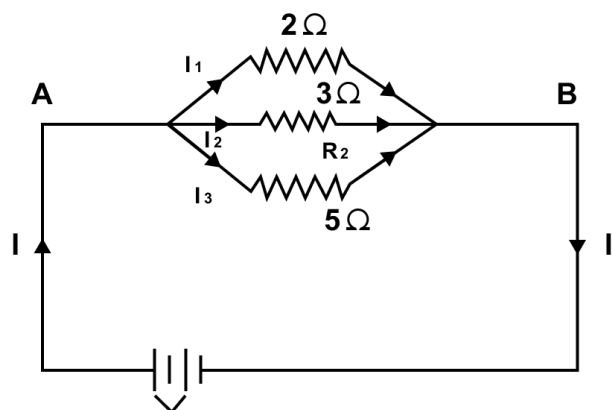In order to get a total resistance less than 1Ω , the three resistors of values 2Ω , 3Ω and 5Ω , should be connected in parallel as shown in the diagram below:



In parallel, if the equivalent resistance is R_p , then

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \Rightarrow \frac{1}{R_p} = \frac{1}{2} + \frac{1}{3} + \frac{1}{5} = \frac{15 + 10 + 6}{30} = \frac{31}{30} \Rightarrow R_p = 0.97\Omega$$


Hence, the three resistors should be connected in parallel and total resistance = 0.97Ω

Question 9

Three resistors each of 2Ω are connected together so that their total resistance is 3Ω . Draw a diagram to show this arrangement and check it by calculation.

Answer

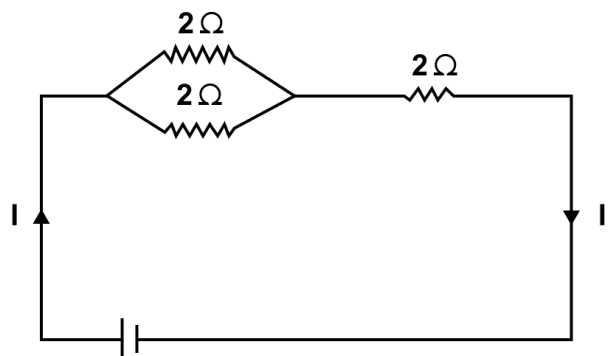When two resistors (2Ω each) in parallel combination are connected to the third resistor (2Ω) in series connection then the resultant resistance is 3Ω . The below diagram shows this arrangement of resistors:



To verify,

Total resistance of two resistors in parallel,

In parallel, if the equivalent resistance is R_p , then

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} \Rightarrow \frac{1}{R_p} = \frac{1}{2} + \frac{1}{2} = \frac{2}{2} \Rightarrow R_p = 1\Omega$$

Hence, $R_p = 1\Omega$

In series connection,


Equivalent resistance = $R_E = R_p + R_3$

$= 1 + 2 = 3\Omega$

Hence, Equivalent resistance = 3Ω

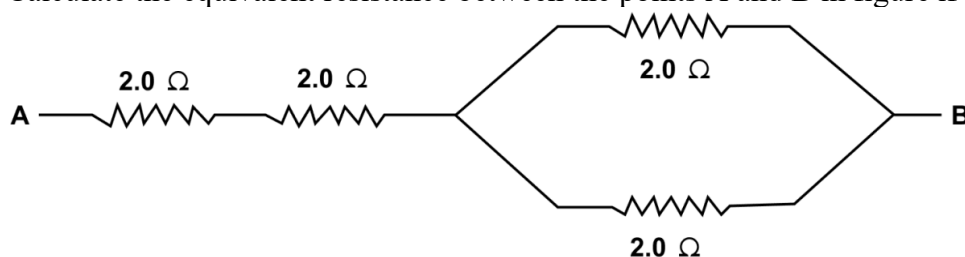Question 10

Calculate the equivalent resistance between the points A and B in figure if each resistance is 2.0Ω .



Answer

Let the resistors be R_1, R_2, R_3, R_4 each of 2.0Ω .

In parallel, if the equivalent resistance is R_p , then

$$\frac{1}{R_p} = \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_p} = \frac{1}{2} + \frac{1}{2} + \frac{1}{R_p} = \frac{2}{2} \Rightarrow R_p = 1\Omega$$

Hence, $R_p = 1 \Omega$

In series connection,

Equivalent resistance = $R_E = R_1 + R_2 + R_p$

$$= 2 + 2 + 1 = 5 \Omega$$

Hence, **Equivalent resistance = 5Ω**

Question 11

A combination consists of three resistors in series. Four similar sets are connected in parallel. If the resistance of each resistor is 2 ohm , find the resistance of the combination.

Answer

Let the four set of resistors be R_1, R_2, R_3, R_4 .

As each set consists of three resistors of 2Ω each in series:

Resistance of each set = $2 + 2 + 2 = 6 \Omega$


As four similar sets of equivalent resistance 6Ω are arranged in parallel, so the equivalent resistance (R_p) will be:

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_p} = \frac{1}{6} + \frac{1}{6} + \frac{1}{6} + \frac{1}{6} + \frac{1}{R_p} = \frac{4}{6} + \frac{1}{R_p} = \frac{4}{6} \Rightarrow R_p = 1.5\Omega$$

Hence, **equivalent resistance = 1.5Ω**

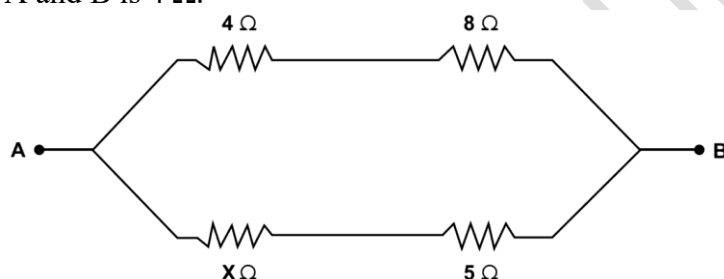Question 12

In the circuit shown below in figure, calculate the value of x if the equivalent resistance between the points A and B is 4Ω .



Answer

In the circuit, there are three parts. In the first part, resistors of 4Ω and 8Ω are connected in series. If the equivalent resistance of this part is R'_s then

$$R'_s = 4 + 8 = 12 \Omega$$

In the second part, resistors of $x \Omega$ and 5Ω are connected in series. If the equivalent resistance of this part is R''_s then

$$R''_s = (x + 5) \Omega$$

In the third part, the two parts of resistance $R'_s = 12 \Omega$ and $R''_s = (x + 5) \Omega$ are connected in parallel. If the equivalent resistance between points A and B is R_p then

$$\frac{1}{R_p} = \frac{1}{R'_s} + \frac{1}{R''_s} = \frac{1}{12} + \frac{1}{x + 5}$$

But it is given that equivalent resistance between points A and B is 4Ω

$$\therefore R_p = 4 \Omega$$


Putting value of R_p in the equation above and solving for x :

$$\begin{aligned} \frac{1}{4} &= \frac{1}{12} + \frac{1}{x + 5} \\ \frac{1}{4} - \frac{1}{12} &= \frac{1}{x + 5} \\ \frac{x + 5 + 12}{12(x + 5)} &= \frac{1}{4} \\ \frac{x + 17}{12(x + 5)} &= \frac{1}{4} \\ 4(x + 17) &= 12(x + 5) \\ 4x + 68 &= 12x + 60 \\ 68 - 60 &= 12x - 4x \\ 8 &= 8x \\ x &= 1 \end{aligned}$$

Hence, the value of $x = 1 \Omega$

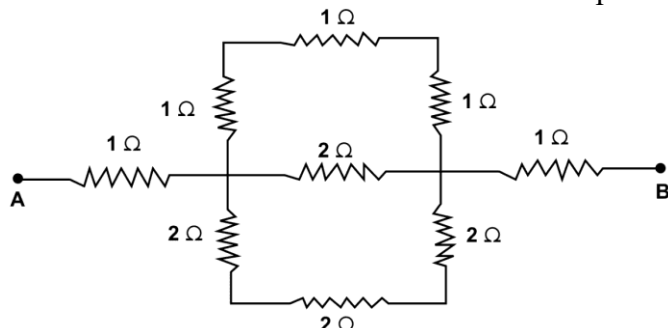Question 13

Calculate the effective resistance between the points A and B in the circuit shown in figure.



Answer

In the circuit, there are four parts. In the first part, three resistors of 1Ω each are connected in series. If the equivalent resistance of this part is R'_s then

$$R'_s = (1 + 1 + 1) \Omega = 3 \Omega$$

In the second part, three resistors of 2Ω each are connected in series. If the equivalent resistance of this part is R''_s then

$$R''_s = (2 + 2 + 2) \Omega = 6 \Omega$$

In the third part, the two parts of resistance $R'_s = 3 \Omega$ and $R''_s = 6 \Omega$ and 2Ω are connected in parallel. If the equivalent resistance is R_p then

$$\frac{1}{R_p} = \frac{1}{R'_s} + \frac{1}{2} + \frac{1}{R''_s} = \frac{1}{3} + \frac{1}{2} + \frac{1}{6} = \frac{2 + 3 + 1}{6} = \frac{6}{6} \Rightarrow R_p = 1 \Omega$$

$$\therefore R_p = 1 \Omega$$

In the fourth part 1Ω , ($R_p = 1 \Omega$) and 1Ω are connected in series in between points A and B.

Hence, the **equivalent resistance is $1 + 1 + 1 = 3 \Omega$**

Question 14

A uniform wire with a resistance of 27Ω is divided into three equal pieces and then they are joined in parallel. Find the equivalent resistance of the parallel combination.

Answer

Given, uniform wire with a resistance of 27Ω is divided into three equal pieces. Hence, resistance of each piece = 9Ω .

Three such pieces are joined in parallel.

In parallel, if the equivalent resistance is R_p , then

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{9} + \frac{1}{9} + \frac{1}{9} = \frac{3}{9} = \frac{1}{3} \Rightarrow R_p = 3 \Omega$$


Hence, **equivalent resistance = 3Ω**

Question 15

A circuit consists of a resistor of 1 ohm in series with a parallel arrangement of resistors of 12 ohm and 6 ohm . Calculate the total resistance of the circuit. Draw a diagram of the arrangement.

Answer

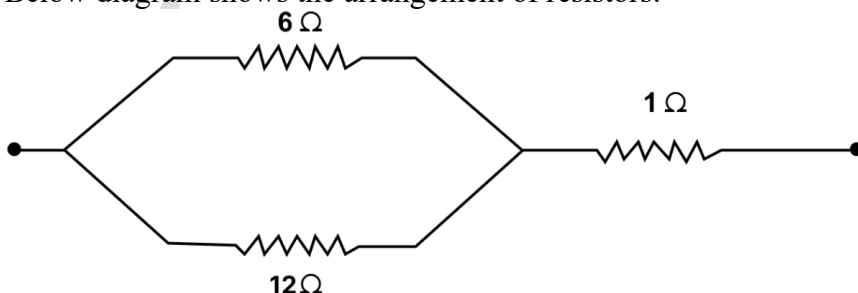Below diagram shows the arrangement of resistors:



In the circuit, there are two parts. In the first part, two resistors of $6\ \Omega$ and $12\ \Omega$ are connected in parallel. If the equivalent resistance is R_p then

$$\frac{1}{R_p} = \frac{1}{12} + \frac{1}{6} = \frac{1+2}{12} = \frac{3}{12} = \frac{1}{4} \Rightarrow R_p = 4\ \Omega$$


Hence, $R_p = 4\ \Omega$

In the second part, $1\ \Omega$ and ($R_p = 4\ \Omega$) are connected in series. If the equivalent resistance is R_s then $R_s = 1 + R_p = 1 + 4 = 5\ \Omega$

Hence, **total resistance of the circuit = $5\ \Omega$**

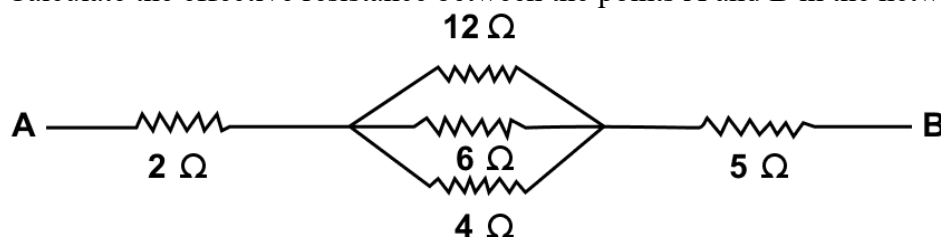Question 16

Calculate the effective resistance between the points A and B in the network shown below in figure.



Answer

In the circuit, there are two parts. In the first part, resistors of $12\ \Omega$, $6\ \Omega$ and $4\ \Omega$ are connected in parallel. If the equivalent resistance of this part is R'_p then

$$\frac{1}{R'_p} = \frac{1}{12} + \frac{1}{6} + \frac{1}{4} = \frac{1+2+3}{12} = \frac{6}{12} = \frac{1}{2} \Rightarrow R'_p = 2\ \Omega$$

Hence, $R'_p = 2\ \Omega$


In the second part, resistors of $2\ \Omega$, ($R'_p = 2\ \Omega$) and $5\ \Omega$ are connected in series. If the equivalent resistance of this part is R_s then

$$R_s = (2 + 2 + 5)\ \Omega = 9\ \Omega$$

Hence, **Effective resistance between A and B = $9\ \Omega$**

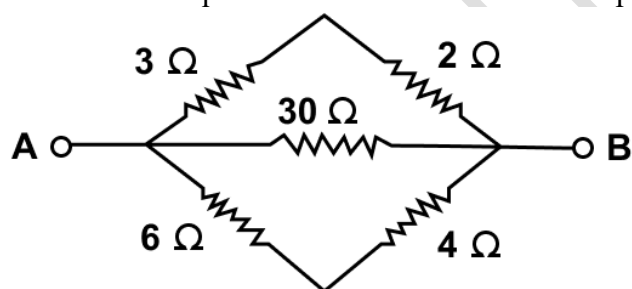Question 17

Calculate the equivalent resistance between the points A and B in figure.



Answer

In the circuit, there are three parts. In the first part, two resistors of $3\ \Omega$, $2\ \Omega$ are connected in series. If the equivalent resistance is R'_s then

$$R'_s = 3 + 2 = 5\ \Omega$$

In the second part, two resistors of $6\ \Omega$, $4\ \Omega$ are connected in series. If the equivalent resistance is R''_s then $R''_s = 6 + 4 = 10\ \Omega$


In the third part R'_s , $30\ \Omega$ and R''_s are connected in parallel. If the equivalent resistance is R_p then

$$\frac{1}{R_p} = \frac{1}{R'_s} + \frac{1}{30} + \frac{1}{R''_s} = \frac{1}{5} + \frac{1}{30} + \frac{1}{10} = \frac{6+1+3}{30} = \frac{10}{30} = \frac{1}{3} \Rightarrow R_p = 3\ \Omega$$

Hence, $R_p = 3\ \Omega$

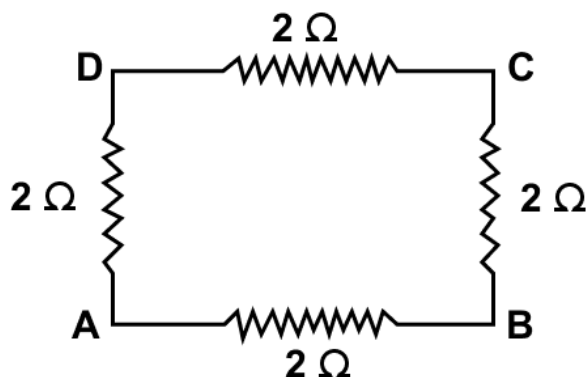Question 18

In the network shown in figure, calculate the equivalent resistance between the points (a) A and B (b) A and C



Answer

In the circuit, there are two parts. In the first part, three resistors of $2\ \Omega$ each are connected in series. If the equivalent resistance of this part is R'_s then

$$R'_s = (2 + 2 + 2)\ \Omega = 6\ \Omega$$

In the second part, the resistance of first part ($R'_s = 6\ \Omega$) and $2\ \Omega$ are connected in parallel. If the equivalent resistance of this part is R_p then

$$\frac{1}{R_p} = \frac{1}{6} + \frac{1}{2} \Rightarrow \frac{1}{R_p} = \frac{1+3}{6} = \frac{4}{6} \Rightarrow R_p = 1.5\ \Omega$$

$$\therefore R_p = 1.5\ \Omega$$

(b) In the circuit, there are three parts. In the first part, two resistors of $2\ \Omega$ each are connected in series. If the equivalent resistance of this part is R'_s then

$$R'_s = (2 + 2)\ \Omega = 4\ \Omega$$

In the second part, two resistors of $2\ \Omega$ each are connected in series. If the equivalent resistance of this part is R''_s then

$$R''_s = (2 + 2)\ \Omega = 4\ \Omega$$


In the third part, the two parts of resistance $R'_s = 4\ \Omega$ and $R''_s = 4\ \Omega$ are connected in parallel. If the equivalent resistance between points A and C is R_p then

$$\frac{1}{R_p} = \frac{1}{4} + \frac{1}{4} \Rightarrow \frac{1}{R_p} = \frac{2}{4} = \frac{1}{2} \Rightarrow R_p = 2\ \Omega$$

$$\therefore \text{Equivalent Resistance between A and C} = 2\ \Omega$$

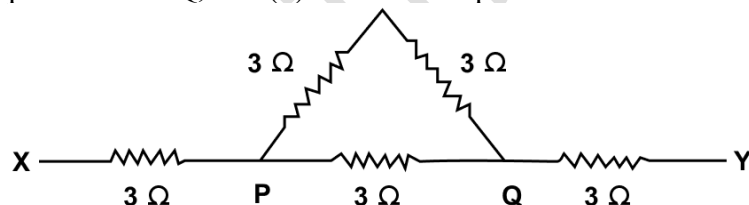Question 19

Five resistors, each of $3\ \Omega$, are connected as shown in figure. Calculate the resistance (a) between the points P and Q, and (b) between the points X and Y.



Answer

(a) In the circuit, there are two parts. In the first part, two resistors of $3\ \Omega$ each are connected in series. If the equivalent resistance of this part is R'_s then

$$R'_s = (3 + 3)\ \Omega = 6\ \Omega$$

In the second part, resistance $R'_s = 6\ \Omega$ and $3\ \Omega$ are connected in parallel. If the equivalent resistance between points P and Q is R_p then

$$\frac{1}{R_p} = \frac{1}{6} + \frac{1}{3} \Rightarrow \frac{1}{R_p} = \frac{1+2}{6} = \frac{3}{6} \Rightarrow R_p = 2\ \Omega$$

$$\therefore \text{Equivalent resistance between the points P and Q} = 2\ \Omega$$

(b) In the circuit, $3\ \Omega$, $R_p = 2\ \Omega$ and $3\ \Omega$ are connected in series. If the equivalent resistance of this part is R_s then

$$R_s = (3 + 2 + 3) \Omega = 8 \Omega$$


\therefore **Equivalent resistance between the points X and Y = 8Ω**

Question 20

Two resistors of 4.0Ω and 6.0Ω are connected (a) in series, (b) in parallel, with a battery of 6.0 V and negligible internal resistance. For each case draw a circuit diagram and calculate the current through the battery.

Answer

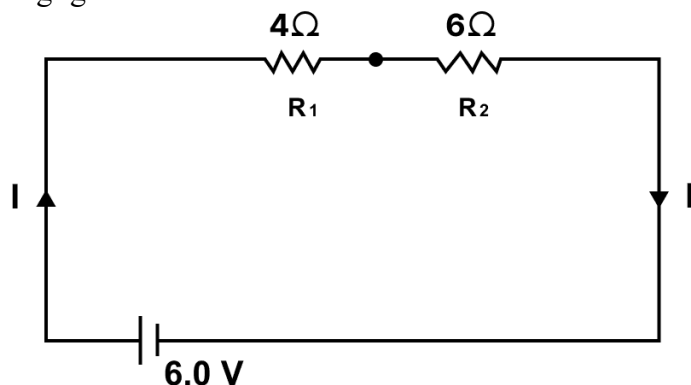(a) Circuit diagram showing two resistors of 4.0Ω and 6.0Ω connected in series with a battery of 6.0 V and negligible internal resistance is shown below:



Given,

Two resistors of 4Ω and 6Ω are connected in series. If the equivalent resistance of this part is R'_s then

$$R'_s = (4 + 6) \Omega = 10 \Omega$$

Potential Difference $V = 6 \text{ V}$

Current $I = ?$

From Ohm's law

$$V = IR$$


Substituting the values in the formula above, we get,

$$6 = I \times 10$$

$$\Rightarrow I = 6 / 10 = 0.6 \text{ A}$$

Hence, **in series, current through the battery = 0.6 A**

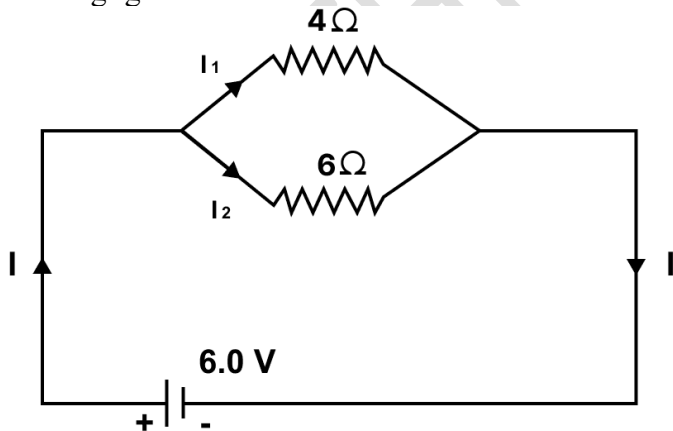(b) Circuit diagram showing two resistors of 4.0Ω and 6.0Ω connected in parallel with a battery of 6.0 V and negligible internal resistance is shown below:



Given,

Two resistors of 4Ω and 6Ω are connected in parallel. If the equivalent resistance of this part is R_p then

$$\frac{1}{R_p} = \frac{1}{4} + \frac{1}{6} = \frac{3 + 2}{12} = \frac{5}{12} \Rightarrow R_p = \frac{12}{5} = 2.4 \Omega$$

Potential Difference $V = 6 \text{ V}$

Current $I = ?$

From Ohm's law

$$V = IR$$

Substituting the values in the formula above, we get,

$$6 = I \times 2.4 \Rightarrow I = 6 / 2.4 = 2.5 \text{ A}$$

Hence, **in parallel, current through the battery = 2.5 A**

Question 21

A resistor of 6Ω is connected in series with another resistor of 4Ω . A potential difference of 20 V is applied across the combination. Calculate (a) the current in the circuit and (b) potential difference across the 6Ω resistor.

Answer

(a) Given,

Two resistors of 6Ω and 4Ω are connected in series. If the equivalent resistance of this part is R'_s then

$$R'_s = (6 + 4) \Omega = 10 \Omega$$

$$\text{Potential Difference } V = 20 \text{ V}$$

$$\text{Current } I = ?$$

From Ohm's law

$$V = IR$$

Substituting the values in the formula above, we get,

$$20 = I \times 10$$

$$\Rightarrow I = 20 / 10 = 2 \text{ A}$$

Hence, **in series, current through the battery = 2 A**

(b) Given,

$$\text{Resistance } R = 6 \Omega$$

$$\text{Potential Difference } V = ?$$

$$\text{Current } I = 2 \text{ A}$$

From Ohm's law

$$V = IR$$

Substituting the values in the formula above, we get,

$$V = 2 \times 6 = 12 \text{ V}$$

Hence, **potential difference = 12 V**

Question 22


Two resistors of resistance 2Ω and 3Ω are connected in parallel to a cell to draw 0.5 A current from the cell.

(a) Draw a labelled diagram of the arrangement.

(b) Calculate the current in each resistor.

Answer

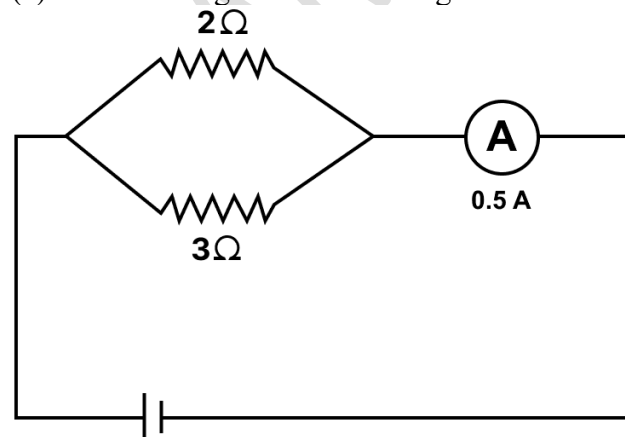(a) Labelled diagram of the arrangement is shown below:



(b) Two resistors of 2Ω and 3Ω are connected in parallel. If the equivalent resistance of this part is R_p then

$$\frac{1}{R_p} = \frac{1}{2} + \frac{1}{3} \frac{1}{R_p} = \frac{3+2}{6} \frac{1}{R_p} = \frac{5}{6} R_p = \frac{6}{5} \Rightarrow R_p = 1.2\Omega$$

Hence, equivalent resistance = 1.2Ω

Current $I = 0.5\text{ A}$

Potential Difference $V = ?$

From Ohm's law

$$V = IR$$

Substituting the values in the formula above, we get,

$$V = 0.5 \times 1.2 = 0.6\text{ V}$$

Current through $2\Omega = ?$

From Ohm's law

$$V = IR$$

Substituting the values in the formula above, we get,

$$0.6 = I \times 2 \Rightarrow I = 0.6 / 2 = 0.3\text{ A}$$

Hence, **current through 2Ω resistor = 0.3 A**

Current through $3\Omega = ?$

From Ohm's law

$$V = IR$$


Substituting the values in the formula above, we get,

$$0.6 = I \times 3 \Rightarrow I = 0.6 / 3 = 0.2\text{ A}$$

Hence, **current through 3Ω resistor = 0.2 A**

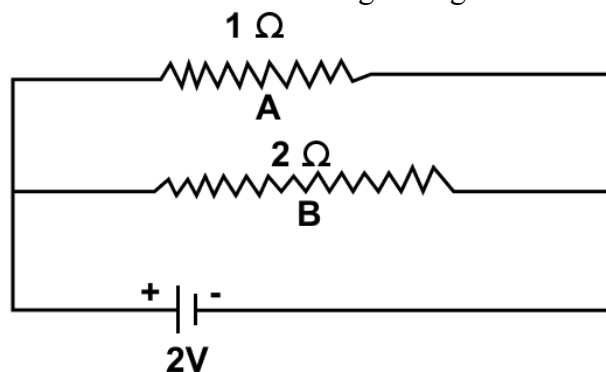Question 23

Calculate the current flowing through each of the resistors A and B in the circuit shown in figure.



Answer

(a) Given,

$$R = 1\Omega$$

$$V = 2\text{ V}$$

Current through $1\Omega = ?$

From Ohm's law

$$V = IR$$

Substituting the values in the formula above, we get,

$$2 = I \times 1$$

$$\Rightarrow I = 2 / 1 = 2\text{ A}$$

Hence, **current through Resistor A = 2 A**

(b) Given,

$$R = 2\Omega$$

$$V = 2\text{ V}$$

Current through $2\Omega = ?$

From Ohm's law

$$V = IR$$

Substituting the values in the formula above, we get,

$$2 = I \times 2$$


$$\Rightarrow I = 2 / 2 = 1 \text{ A}$$

Hence, **current through Resistor B = 1 A**

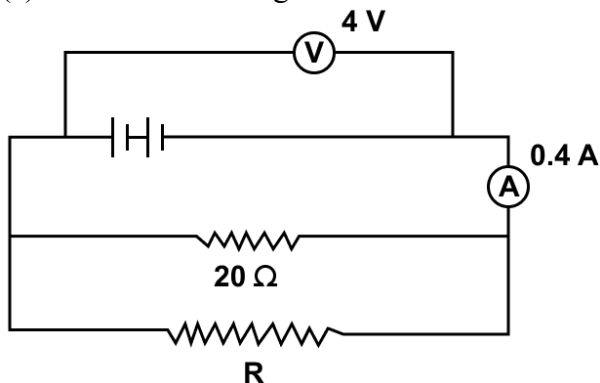Question 24

In figure, calculate —

- the total resistance of the circuit,
- the value of R , and
- the current flowing in R



Answer

(a) Given,

$$V = 4 \text{ V}$$

$$I = 0.4 \text{ A}$$

From Ohm's law

$$V = IR$$

$$4 = 0.4 \times R$$

$$\Rightarrow R = 4 / 0.4 = 10 \Omega$$

Hence, **total resistance of the circuit = 10 Ω**

(b) As total resistance of the circuit is equal to 10 Ω and the two resistors R and 20 Ω are connected in parallel, hence we get,

$$\frac{1}{10} = \frac{1}{R} + \frac{1}{20} \quad \frac{1}{R} = \frac{1}{10} - \frac{1}{20} = \frac{2-1}{20} = \frac{1}{20} \quad R = 20\Omega$$

Hence, **the value of $R = 20 \Omega$**

(c) current flowing in $R = ?$

$$V = 4 \text{ V}$$

$$R = 20 \Omega$$

$$I = ?$$

From Ohm's law

$$V = IR$$

$$\Rightarrow 4 = I \times 20$$

$$\Rightarrow I = 4 / 20 = 1 / 5 = 0.2 \text{ A}$$

Hence, **the current flowing in $R = 0.2 \text{ A}$**

Question 25

A particular resistance wire has a resistance of 3.0 ohm per meter. Find —

- The total resistance of three lengths of this wire each 1.5 m long, joined in parallel.
- The potential difference of the battery which gives a current of 2.0 A in each of the 1.5 m length when connected in parallel to the battery (assume that resistance of the battery is negligible).
- The resistance of 5 m length of a wire of the same material, but with twice the area of cross section.

Answer

(a) Resistance of 1 m of wire = 3 Ω.

Resistance of 1.5 m of wire = $3 \times 1.5 = 4.5 \Omega$. As three such wires are joined in parallel and if the equivalent resistance of this part is R_p then

$$\frac{1}{R_p} = \frac{1}{4.5} + \frac{1}{4.5} + \frac{1}{4.5} \Rightarrow \frac{1}{R_p} = \frac{3}{4.5} \Rightarrow R_p = 1.5 \Omega$$

Hence, **total resistance of circuit = 1.5Ω**

(b) $I = 2 \text{ A}$

From Ohm's Law

$$V = IR$$

Substituting the values in the formula above we get,

$$V = 2 \times 4.5 = 9 \text{ V}$$

Hence, **potential difference = 9 V**

(c) $R = 3 \Omega$ for 1 meter wire

Therefore, for 5 m

$$R = 3 \times 5 = 15 \Omega$$

Here the area is twice and resistance is inversely proportional to area.

Thus, resistance becomes half

$$R = 15 / 2 = 7.5 \Omega$$

Hence, **resistance = 7.5Ω**

Question 26

A cell supplies a current of 1.2 A through two resistors each of 2Ω connected in parallel. When the resistors are connected in series, it supplies a current of 0.4 A . Calculate (i) the internal resistance and (ii) e.m.f. of the cell.

Answer

(i) Given,

Two resistors each of 2Ω connected in parallel. If the equivalent resistance of this part is R_p then

$$\frac{1}{R_p} = \frac{1}{2} + \frac{1}{2} \Rightarrow \frac{1}{R_p} = \frac{2}{2} \Rightarrow R_p = 1 \Omega$$

Hence, equivalent resistance $R_p = 1 \Omega$

Given,

$$I = 1.2 \text{ A}$$

From relation,

$$\epsilon = I(R + r)$$

$$\epsilon = 1.2(1 + r)$$

$$\epsilon = 1.2 + 1.2r \quad \text{[Equation 1]}$$

When the resistors are connected in series, it supplies a current of 0.4 A ,

If the equivalent resistance of this part is R_s then

$$R_s = 2 + 2 = 4 \Omega$$

Hence, equivalent resistance $R_s = 4 \Omega$

Given, $I = 0.4 \text{ A}$

From relation,

$$\epsilon = I(R + r)$$

$$\epsilon = 0.4(4 + r)$$

$$\epsilon = 1.6 + 0.4r \quad \text{[Equation 2]}$$

Equating 1 and 2, we get,

$$1.2 + 1.2r = 1.6 + 0.4r$$

$$\Rightarrow 1.2r - 0.4r = 1.6 - 1.2$$

$$\Rightarrow 0.8r = 0.4$$

$$\Rightarrow r = \frac{0.4}{0.8}$$

$$\Rightarrow r = 0.5 \Omega$$

Hence, **Internal resistance $r = 0.5 \Omega$**

(ii) Substituting the value in equation 1 we get,

$$\varepsilon = 1.2(1 + r)$$

$$= 1.2(1 + 0.5)$$

$$= 1.2 \times 1.5$$

$$= 1.8 \text{ V}$$

Hence, **e.m.f. of the cell = 1.8 V**

Question 27

A battery of e.m.f. 16 V and internal resistance 2Ω is connected to two resistors 3Ω and 6Ω connected in parallel. Find (a) the current through the battery (b) p.d. between the terminals of the battery (c) the current in 3Ω resistor (d) the current in 6Ω resistor.

Answer

(a) Given,

$$\text{e.m.f.} = 16 \text{ V}$$

$$\text{internal resistance } r = 2 \Omega$$

$$\text{current through battery} = ?$$

If R_p is the equivalent resistance of resistors 3Ω and 6Ω connected in parallel, then

$$\frac{1}{R_p} = \frac{1}{3} + \frac{1}{6} = \frac{2 + 1}{6} = \frac{3}{6} = \frac{1}{2} \Rightarrow R_p = 2 \Omega$$

From relation,

$$\varepsilon = I(R + r)$$

Substituting the value in the formula above we get,

$$16 = I(2 + 2)$$

$$\Rightarrow 16 = I \times 4 \Rightarrow I = 16 / 4 = 4 \text{ A}$$

Hence, **current through the battery = 4 A**

(b) Potential difference between the terminals of the battery = ?

Using Ohm's law

$$V = IR$$

$$R = 2 \Omega$$

$$I = 4 \text{ A}$$

Substituting the values in the formula above we get,

$$V = 4 \times 2 = 8 \text{ V}$$

Hence, **potential difference between the terminals of the battery = 8 V**

(c) Current in 3Ω resistor = ?

Using Ohm's law

$$V = IR$$

$$R = 3 \Omega$$

$$V = 8 \text{ V}$$

$$I = ?$$

Substituting the values in the formula above we get,

$$8 = I \times 3$$

$$I = \frac{8}{3}$$

$$\Rightarrow I = 2.66 \text{ A}$$

Hence, **current in 3Ω resistor is 2.66 A**

(d) Current in 6Ω resistor = ?

Using Ohm's law

$$V = IR$$

$$R = 6 \Omega$$

$$V = 8 \text{ V}$$

$$I = ?$$

Substituting the values in the formula above we get,

$$8 = I \times 6$$


$$\Rightarrow I = 8 / 6 = 1.333 \text{ A}$$

Hence, **current in 6 Ω resistor is 1.34 A**

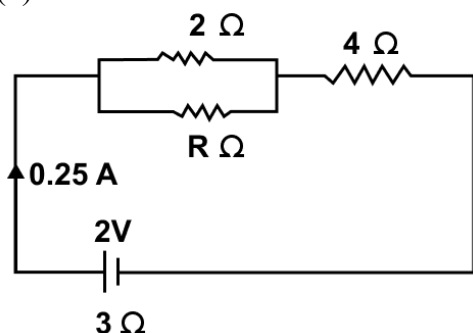Question 28

The circuit diagram in figure shows three resistors 2 Ω , 4 Ω and R Ω connected to a battery of e.m.f. 2V and internal resistance 3 Ω . If main current of 0.25 A flows through the circuit, find —

- the p.d. across the 4 Ω resistor
- the p.d. across the internal resistance of the cell,
- the p.d. across the R Ω or 2 Ω resistor, and
- the value of R.



Answer

(a) Given,
resistor = 4 Ω

$$I = 0.25 \text{ A}$$

the p.d. across the 4 Ω resistor (V) = ?

Using Ohm's law

$$V = IR$$

Substituting the values in the formula above we get,

$$V = 0.25 \times 4 = 1 \text{ V}$$

Hence, **the p.d. across the 4 Ω resistor (V) = 1 V**

(b) Given,

internal resistance = 3 Ω

$$I = 0.25 \text{ A}$$

the p.d. across the internal resistance of the cell = ?

Using Ohm's law

$$V = IR$$

Substituting the values in the formula above we get,

$$V = 0.25 \times 3 = 0.75 \text{ V}$$

Hence, **the p.d. across the internal resistance (V) = 0.75 V**

(c) Potential difference across R Ω or 2 Ω

$$V = V_{\text{net}} - V_{\text{across } 4 \Omega} - V_{\text{across } 3 \Omega}$$

Hence, we get,

$$V = 2 - 1 - 0.75 = 0.25 \text{ V}$$

(d) The p.d. across resistor of R Ω = 0.25 V

Let the equivalent resistance of the resistors of 2 Ω and R Ω connected in parallel be R'_p

$$\frac{1}{R'_p} = \frac{1}{R} + \frac{1}{2} \Rightarrow \frac{1}{R'_p} = \frac{2+R}{2R} \Rightarrow R'_p = \frac{2R}{2+R}$$

Using Ohm's law

$$V = IR$$

$$0.25 = 0.25 \times R'_p$$

Substituting the value of R'_p from above:

$$0.25 = 0.25 \times \left(\frac{2R}{2+R}\right)$$

$$\Rightarrow \frac{2R}{2+R} = 1$$

$$\Rightarrow 2R = 2 + R$$

$$\Rightarrow 2R - R = 2$$


$$\Rightarrow R = 2 \Omega$$

Hence, value of $R = 2 \Omega$

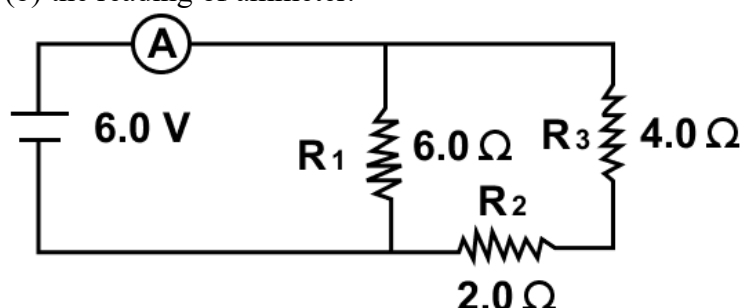Question 29

Three resistors of 6.0Ω , 2.0Ω and 4.0Ω are joined to an ammeter A and a cell of e.m.f. 6.0 V as shown in figure. Calculate —

- the effective resistance of the circuit, and
- the reading of ammeter.



Answer

(a) In the circuit, there are two parts. In the first part, resistors of 2.0 and 4.0Ω are connected in series. If the equivalent resistance of this part is R_s then

$$R_s = 2 + 4 = 6 \Omega$$

In the second part, $R_s = 6.0$ and resistor of 6.0Ω are connected in parallel. If the equivalent resistance of this part is R_p then

$$\frac{1}{R_p} = \frac{1}{6} + \frac{1}{6} = \frac{1+1}{6} = \frac{2}{6} \Rightarrow R_p = \frac{6}{2} = 3.0 \Omega$$

Hence, the effective resistance of the circuit = 3Ω

(b) The reading of ammeter = ?

$$R = 3 \Omega$$

$$V = 6.0 \text{ V}$$

Using Ohm's law,

$$V = IR$$

Substituting the values in the formula above we get,

$$6 = I \times 3$$


$$\Rightarrow I = 6 / 3 = 2 \text{ A}$$

Hence, the reading of ammeter = 2 A

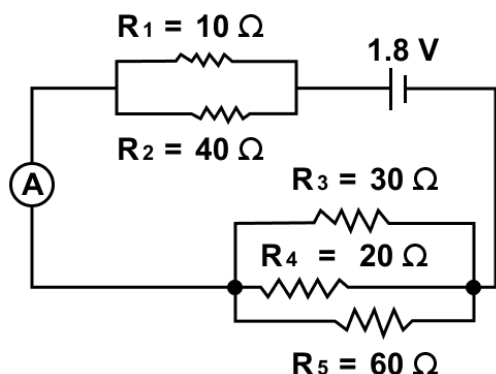Question 30

The diagram below in figure shows the arrangement of five different resistances connected to a battery of e.m.f. 1.8 V . Calculate —

- the total resistance of the circuit, and
- the reading of ammeter A.



Answer

(a) In the circuit, there are three parts. In the first part, resistors of $10\ \Omega$ and $40\ \Omega$ are connected in parallel. If the equivalent resistance of this part is R'_p then

$$\frac{1}{R'_p} = \frac{1}{10} + \frac{1}{40} \Rightarrow \frac{1}{R'_p} = \frac{4+1}{40} \Rightarrow \frac{1}{R'_p} = \frac{5}{40} \Rightarrow R'_p = \frac{40}{5} = 8\ \Omega$$

In the second part, resistors of $30\ \Omega$, $20\ \Omega$ and $60\ \Omega$ are connected in parallel. If the equivalent resistance of this part is R''_p then

$$\frac{1}{R''_p} = \frac{1}{30} + \frac{1}{20} + \frac{1}{60} \Rightarrow \frac{1}{R''_p} = \frac{2+3+1}{60} \Rightarrow \frac{1}{R''_p} = \frac{6}{60} \Rightarrow R''_p = \frac{60}{6} = 10\ \Omega$$

In the third part, resistors R'_p and R''_p are connected in series. If the equivalent resistance of this part is R_s then

$$R_s = 8 + 10 = 18\ \Omega$$

Hence, **the total resistance of the circuit = $18\ \Omega$**

(b) Given,

e.m.f. = $1.8\ \text{V}$

effective resistance of the circuit = $18\ \Omega$

$I = ?$

From Ohm's law

$V = IR$

Substituting the values in the formula above, we get,

$$1.8 = I \times 18$$


$$\Rightarrow I = \frac{1.8}{18}$$

$$\Rightarrow I = 0.1\ \text{A}$$

Hence, **the reading of ammeter = $0.1\ \text{A}$**

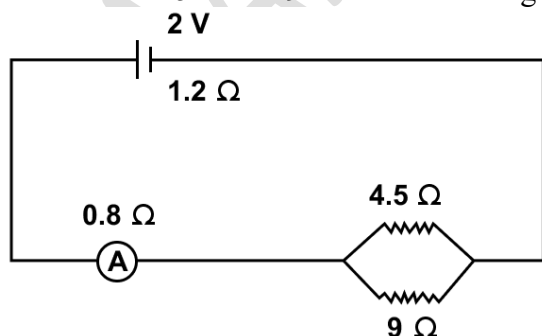Question 31

A cell of e.m.f. $2\ \text{V}$ and internal resistance $1.2\ \Omega$ is connected to an ammeter of resistance $0.8\ \Omega$ and two resistors of $4.5\ \Omega$ and $9\ \Omega$ as shown in figure.



Find —

(a) the reading of the ammeter,

(b) the potential difference across the terminals of the cell, and

(c) the potential difference across the 4.5Ω resistor.

Answer

(a) Given,

e.m.f. = 2V

$I = ?$

In the circuit, there are two parts. In the first part, resistors of 4.5Ω and 9Ω are connected in parallel. If the equivalent resistance of this part is R_p then

$$\frac{1}{R_p} = \frac{1}{4.5} + \frac{1}{9} \Rightarrow \frac{1}{R_p} = \frac{2}{9} \Rightarrow R_p = \frac{9}{2} = 4.5 \Omega$$

In the second part, 1.2Ω , 0.8Ω and $R_p = 3 \Omega$ are connected in series. If the equivalent resistance of this part is R_s then

$$R_s = 1.2 + 0.8 + 3 = 5 \Omega$$

Hence, **the effective resistance of the circuit = 5Ω**

Using Ohm's law,

$$V = IR$$

$$2 = I \times 5$$

$$\Rightarrow I = \frac{2}{5}$$

$$\Rightarrow I = 0.4 \text{ A}$$

Hence, **the reading of the ammeter = 0.4 A**

(b) The potential difference across the ends of the cells = ?

$$\varepsilon = 2 \text{ V}$$

$$I = 0.4 \text{ A}$$

$$r = 1.2 \Omega$$

From relation,

$$\text{Voltage (V)} = \varepsilon - Ir$$

Substituting the values in the formula we get,

$$V = 2 - (0.4 \times 1.2)$$

$$\Rightarrow V = 2 - 0.48$$

$$\Rightarrow V = 1.52 \text{ V}$$

Hence, **potential difference across the terminals of the cell = 1.52 V**

(c) The potential difference across the 4.5Ω resistor = ?

Current flowing is $I = 0.4 \text{ A}$. Now the current I divides in two parts. Let the current in 4.5Ω resistor be I_1 and in 9Ω resistor be I_2 .

$$\text{So } I = I_1 + I_2$$

$$\text{and } I_1 \times 4.5 = I_2 \times 9$$

On solving,

$$I_1 = \frac{9}{4.5 + 9} \times I = \frac{9}{13.5} \times 0.4 = 0.2667$$

p.d. across the 4.5Ω resistor

$$= I_1 \times 4.5 = 0.2667 \times 4.5 = 1.2 \text{ V}$$

Alternate Method:

$$V_{4.5\Omega} = V_{\text{cell}} - V_{\text{ammeter}}$$

$$V_{4.5\Omega} = 1.52 - IR_{\text{ammeter}} = 1.52 - (0.4 \times 0.8) = 1.52 - 0.32 = 1.2 \text{ V}$$

Hence, **p.d. across the 4.5Ω resistor = 1.2 V**

Exercise 8(C) — Multiple Choice Type

Question 1

The electrical energy supplied by a source is given by:

1. $W = QV$
2. $W = VIt$
3. $W = I^2Rt$

4. All of the above

Answer

All of the above

Reason — We know, $W = QV$

As, $Q = It$

Hence, substituting we get

$W = VIt$

And By Ohm's Law : $V = IR$

Hence, substituting we get

$W = (IR)It = I^2Rt$

Question 2

1 WH is equal to :

1. 3600 J
2. 360 J
3. 36 J
4. 3.6 J

Answer

3600 J

Reason — 1 watt-hour = 1 watt x 1 hour = 1 W x (60 x 60 s) = 3600 J

Hence, 1 WH = 3600 J

Question 3

The amount of heat produced in a wire on passing a current through it depends on:

1. the resistance of wire
2. the square root of current I passing through the wire.
3. the time for which current is passed.
4. Both (1) and (3)

Answer

Both (1) and (3)

Reason — The amount of heat produced in a wire on passing current through it, depends on the following three factors.

1. **The amount of current passing through the wire** — The amount of heat H produced in a wire is directly proportional to the square of current I passing through the wire, i.e., $H \propto I^2$
2. **The resistance of wire** — The amount of heat H produced in the wire is directly proportional to the resistance R of the wire, i.e., $H \propto R$.
3. **The time for which current is passed in the wire** — The amount of heat H produced in a wire is directly proportional to the time t for which current is passed in the wire i.e., $H \propto t$

Question 4

An electrical appliance has a rating 100 W, 120 V. The resistance of element of appliance when in use is —

1. 1.2 Ω
2. 144 Ω
3. 120 Ω
4. 100 Ω

Answer

144 Ω

Reason — Resistance of an electrical appliance (rating 100 W, 120 V) is :

$$R_A = \frac{V^2}{P_A}$$

Substituting the values in the formula above we get,

$$R_A = \frac{120^2}{100} \Rightarrow R_A = 144\Omega$$

Hence, resistance of an electrical appliance = 144Ω

Question 5

A bulb is rated 100 W-220 V. It is being used at 110 V supply. The power consumed by bulb is:

1. 100 W
2. half of 100 W
3. nearly 25 W
4. none of the above

Answer

nearly 25 W

Reason — Given,

Power (P) = 100 W

Voltage (V) = 220 V

We know that,

Power (P) = VI

Substituting the values in the formula above, we get,

$$100 = 220 \times I$$

$$\Rightarrow I = \frac{100}{220}$$

$$\Rightarrow I = 0.45 \text{ A}$$

Hence, current through the lamp = **0.45 A**

Power consumed when voltage is 110 V = ?

$$\text{Resistance of lamp (R)} = \frac{V^2}{P}$$

Substituting the values in the formula, we get,

$$R = \frac{220^2}{100} \Rightarrow R = 484 \Omega$$

From relation,

$$P = \frac{V^2}{R}$$

Substituting the values in the formula, we get,

$$P = \frac{110^2}{484} \Rightarrow P = 25 \text{ W}$$

Hence, power consumed is **25 W**

Exercise 8(C) — Very Short Questions

Question 1

Write an expression for the electrical energy spent in flow of current through an electrical appliance in terms of current, resistance and time.

Answer

The expression for electrical energy spent in flow of current through an electrical appliance in terms of current, resistance and time is:

$$W = I^2 R t$$

Question 2

Write an expression for the electrical power spent in flow of current through a conductor in terms of (a) resistance and potential difference, (b) current and resistance.

Answer

(a) Expression for electrical power spent in flow of current through a conductor in terms of resistance and potential difference is —

$$W = \frac{V^2}{R}$$

(b) Expression for electrical power spent in flow of current through a conductor in terms of current and resistance is —

$$W = I^2 R$$

Question 3

State the S.I. unit of electrical power.

Answer

The S.I. unit of electrical power is **volt x ampere (VA) or watt (W) or $J s^{-1}$**

One watt is the electric power consumed when a current of 1 ampere flows through a circuit having a potential difference of 1 volt.

Question 4

Name the physical quantity which is measured in (i) kW, (ii) kWh. (iii) Wh

Answer

(i) The physical quantity measured in kW is **electrical power**.

(ii) The physical quantity measured in kWh is **electrical energy**. kWh is commercial unit of electrical energy.

(iii) The physical quantity measured in Wh is **electrical energy**. Wh is commercial unit of electrical energy.

Question 5

Complete the following —


$$(a) 1 \text{ kWh} = \frac{1 \text{ volt} \times 1 \text{ ampere} \times \dots \dots}{1000} \quad (b) 1 \text{ kWh} = \dots \dots \text{ J}$$

Answer

$$(a) 1 \text{ kWh} = \frac{1 \text{ volt} \times 1 \text{ ampere} \times 1 \text{ hour}}{1000} \quad (b) 1 \text{ kWh} = 3.6 \times 10^6 \text{ J}$$

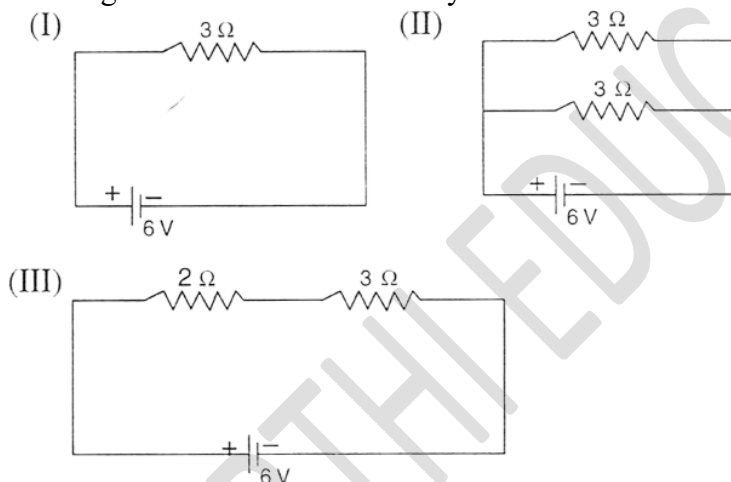Question 6

You are given three circuits. Identify the circuit with the minimum dissipation of heat.



Answer

For circuit (I) :

Net Resistance (R) = 3Ω

Voltage (V) = 6 V

$$\text{Heat Dissipated} = P = \frac{V^2}{R} = \frac{6 \times 6}{3} = \frac{36}{3} = 12 \text{ W} \dots \dots (1)$$

For circuit (II) :

As resistances are in parallel combination and also have equal value then

$$\frac{1}{R} = \frac{1}{3} + \frac{1}{3} = \frac{2}{3}$$

So, net resistance (R) = $\frac{3}{2} \Omega$

Voltage (V) = 6V

$$\text{Heat Dissipated} = P = \frac{V^2}{R} = \frac{6 \times 6}{\frac{3}{2}} = \frac{36 \times 2}{3} = 12 \times 2 = 24 \text{ W} \dots \dots (2)$$

For circuit (III) :

As resistances are in series combination then

$$R = 2 + 3 = 5 \Omega$$

So, net resistance (R) = 5 Ω

Voltage (V) = 6V

$$\text{Heat Dissipated} = P = \frac{V^2}{R} = \frac{6 \times 6}{5} = \frac{36}{5} = 7.2 \text{ W} \dots\dots\dots (3)$$

From (1), (2) and (3) it is clearly visible that **in circuit (iii) heat dissipation is minimum.**

Exercise 8(C) — Short Questions

Question 1

Electrical power P is given by the expression $P = \frac{(Q \times V)}{\text{time}}$.

(a) What do the symbols Q and V represent?

(b) Express the power P in terms of current and resistance explaining the meaning of symbols used there in.

Answer

(a) In the expression,

$$P = \frac{Q \times V}{\text{time}}$$

Symbol **Q** represents charge and the symbol **V** represents voltage.

(b) The expression for power P in terms of current and resistance is:

$$P = I^2 R$$

where,

I represents current and

R represents resistance.

Question 2

Name the S.I. unit of electrical energy. How is it related to Wh?

Answer

The S.I. unit of electrical energy is **Joule**.

The relation between Wh and Joule is as follows —

$$1 \text{ Wh} = 3600 \text{ J}$$

Question 3

Explain the meaning of the statement 'the power of an appliance is 100 W'.

Answer

The statement 'the power of an appliance is 100 W' means that 100 J of electrical energy is consumed by the appliance in 1 second.

Question 4

(i) State and define the household unit of electricity.

(ii) What is the voltage of the electricity that is generally supplied to a house?

(iii) What is consumed while using different electrical appliances, for which electricity bills are paid?

Answer

(i) The household unit of electricity is **Kilowatt hour (kWh)**.

One kilowatt-hour (kWh) is the electrical energy consumed by an electrical appliance of power 1 kilowatt when it is used for 1 hour.

(ii) The voltage of the electricity that is generally supplied to a house is **220 volt**.

(iii) The **electrical energy** is consumed by various appliances in our houses (or industries) and its cost is paid to the electrical company.

Question 5

Define the term kilowatt-hour and state its value in S.I. unit.

Answer

One kilowatt-hour (kWh) is the electrical energy consumed by an electrical appliance of power 1 kilowatt when it is used for 1 hour.

Value of kilowatt-hour (kWh) in S.I. unit is —

1 kWh = 3.6×10^6 J

Question 6

How do kilowatt and kilowatt-hour differ?

Answer

Kilowatt is the unit of **electrical power**. i.e., one kilowatt is the electric power consumed when a current of 1 ampere flows through a circuit having a potential difference of 1 volt.

Kilowatt-hour is the unit of **electrical energy** i.e., One kilowatt - hour (kwh) is the **electrical energy** consumed by an electrical appliance of power 1 kilowatt when it is used for 1 hour.

Question 7

What do you mean by power rating of an electrical appliance? How do you use it to calculate (a) the resistance of the appliance and (b) the safe limit of the current in it, while in use ?

Answer

An electrical appliance such as electric heater, geyser etc is rated with its power and voltage.

For example, an electric bulb is rated as 100 W - 220 V. It means that if the bulb is lighted on a 220 V supply, the electric power consumed by it is 100 W (i.e., 100 J of electric energy is consumed by the bulb in 1 s).

(a) Resistance of element of appliance while in use is —

$$R = \frac{V^2}{P}$$

(b) The safe limit of current in it, while in use is —

$$I = \frac{P}{V}$$

If current exceeds this value, the power supplied at voltage V will exceed the rated power of the appliance and the appliance may get damaged. So this value of current is called the safe current which can flow through the appliance at voltage V.

Question 8

An electric bulb is rated '100 W, 250 V'. What information does this convey ?

Answer

When an electric bulb is rated '100 W, 250 V' it means that if the bulb is lighted on a 250 V supply, the electric power consumed by it is 100 W (i.e., 100 J of electrical energy is consumed by the bulb in 1 s).

Exercise 8(C) — Long Questions

Question 1

List the names of three electrical gadgets used in your house. Write their power, voltage rating and approximate time for which each one is used in a day. Hence find the electrical energy consumed by each in a month of 30 days.

Answer

Appliance	Power (in kilowatt)	Voltage (V)	Time (t)	Electrical energy ($E = P \times t$) in (kWh)
Fluorescent tube	0.04	220	6	0.24
Television set	0.12	220	3	0.36
Room heater	1	220	2	2

(i) Energy consumed by **fluorescent tube** in one day = 0.24 kWh

Hence, energy consumed in 30 days = $0.24 \times 30 = 7.2$ kWh.

(ii) Energy consumed by **television set** in one day = 0.36 kWh

Hence, energy consumed in 30 days = $0.36 \times 30 = 10.8$ kWh.

(iii) Energy consumed by **room heater** in one day = 2 kWh

Hence, energy consumed in 30 days = $2 \times 30 = 60$ kWh.

Question 2

Two lamps, one rated 220 V, 50 W and the other rated 220 V, 100 W, are connected in series with mains of voltage 220 V. Explain why does the 50 W lamp consume more power.

Answer

Resistance of lamp A (rating 220 V, 50 W) is —

$$R_A = \frac{V^2}{P_A}$$

Substituting the values in the formula above we get,

$$R_A = \frac{220^2}{50} \Rightarrow R_A = 968\Omega$$

Resistance of lamp B (rating 220 V, 100 W) is —

$$R_B = \frac{V^2}{P_B}$$

Substituting the values in the formula above we get,

$$R_B = \frac{220^2}{100} \Rightarrow R_B = 484\Omega$$

From formula, we get, $P = I^2 R$

As we observe that $R_A > R_B$ and same current is flowing in both the lamps as both are connected in series therefore $P_A > P_B$. Hence, 50 W lamp consumes more power than 100 W lamp.

Question 3

Name the factors on which the heat produced in a wire depends when current is passed in it, and state how does it depend on the factors stated by you.

Answer

The amount of heat produced in a wire on passing current through it, depends on the following three factors.

1. **The amount of current passing through the wire** — The amount of heat H produced in a wire is directly proportional to the square of current I passing through the wire, i.e., $H \propto I^2$
2. **The resistance of wire** — The amount of heat H produced in the wire is directly proportional to the resistance R of the wire, i.e., $H \propto R$.
3. **The time for which current is passed in the wire** — The amount of heat H produced in a wire is directly proportional to the time t for which current is passed in the wire i.e., $H \propto t$

Exercise 8(C) — Numericals

An electric bulb of resistance 500Ω draws current 0.4 A from the source. Calculate: (a) the power of bulb and (b) the potential difference at its end.

Answer

(a) Given,

Resistance (R) = 500Ω

Current (I) = 0.4 A

Power = ?

From Ohm's law:

$$V = IR$$

Substituting the values in the formula above, we get,

$$V = 0.4 \times 500 = 200 \text{ V}$$

$$\text{Power (P)} = VI$$

Substituting the values in the power formula we get,

$$P = 200 \times 0.4 = 80 \text{ W}$$

Hence, **the power of bulb = 80 W**

(b) The **potential difference at its end = 200 V**

Question 2

A current of 3 A is passed through a coil of resistance $75\ \Omega$ for 2 minutes. (a) How much heat energy is produced? (b) How much charge is passed through the resistance ?

Answer

(a) Given,

Current (I) = 3 A

Resistance (R) = $75\ \Omega$

Time (t) = 2 min = 120 s

Heat produced = ?

Using

$$H = I^2 R t$$

Substituting the values in the formula above, we get,

$$H = 3^2 \times 75 \times 120$$

$$\Rightarrow H = 81000\text{ J}$$

Hence, **heat energy produced = 81000 J**

(b) Charge passed through the resistance = ?

From relation,

$$Q = It$$

Substituting the values in the formula above we get,

$$Q = 3 \times 120$$

$$\Rightarrow Q = 360\text{ C}$$

Hence, **charge passed through the resistance = 360 C**

Question 3

Calculate the current through a 60 W lamp rated for 250 V. If the line voltage falls to 200 V, how is power consumed by the lamp affected?

Answer

Given,

Power (P) = 60 W

Voltage (V) = 250 V

We know that,

$$\text{Power (P)} = VI$$

Substituting the values in the formula above, we get,

$$60 = 250 \times I$$

$$\Rightarrow I = \frac{60}{250}$$

$$\Rightarrow I = 0.24\text{ A}$$

Hence, **current through the lamp = 0.24 A**

Power consumed when voltage is 200 V = ?

$$\text{Resistance of lamp (R)} = \frac{V^2}{P}$$

Substituting the values in the formula, we get,

$$R = \frac{250^2}{60} \Rightarrow R = 1041.6\ \Omega$$

From relation,

$$P = \frac{V^2}{R}$$

Substituting the values in the formula, we get,

$$P = \frac{200^2}{1041.6} \Rightarrow P = 38.4\text{ W}$$

Hence, **power consumed reduces to 38.4 W**

Question 4

An electric bulb is rated '100 W, 250 V'. How much current will the bulb draw if connected to a 250 V supply ?

Answer

Given,

Power (P) = 100 W

Voltage (V) = 250 V

From relation,

Power (P) = VI

Substituting the values in the formula above, we get,

$$100 = 250 \times I$$

$$\Rightarrow I = \frac{100}{250}$$

$$\Rightarrow I = 0.4 \text{ A}$$

Hence, **current drawn = 0.4 A**

Question 5

An electric bulb is rated '220 V, 100 W'. (a) What is its resistance? (b) What safe current can be passed through it?

Answer

(a) Given,

P = 100 W

V = 220 volt

We know that,

$$\text{Power } P = \frac{V^2}{R}$$

Substituting the values in the formula above, we get,

$$100 = \frac{220^2}{R}$$

$$\Rightarrow R = \frac{220^2}{100}$$

$$\Rightarrow R = 484 \Omega$$

Hence, **resistance of electric bulb = 484 Ω**

(b) From relation $P = VI$

$$\text{Safe current } I = \frac{P}{V}$$

Substituting the value we get,

$$I = \frac{100}{220}$$

$$\Rightarrow I = 0.45 \text{ A}$$

Hence, **safe current limit = 0.45 A**

Question 6

A bulb of power 60 W is used for 12.5 h each day for 30 days. Calculate the electrical energy consumed.

Answer

Given,

Power (P) = 60 W

time (t) = 12.5 h for 30 days

As energy consumed (E) = P \times t

$$E = 60 \times 12.5$$

$$\Rightarrow E = 750 \text{ Wh}$$

Hence, **electrical energy consumed in one day = 750 Wh**

Electrical energy consumed in 30 days = ?

$$E = 750 \times 30$$

$$E = 22500 \text{ Wh}$$

$$E = 22.5 \text{ kWh}$$

Hence, **electrical energy consumed in 30 days = 22.5 kWh**

Question 7

An electric press is rated '750 W, 230 V'. Calculate the electrical energy consumed by the press in 16 hours.

Answer

Given,

Power (P) = 750 W

time (t) = 16 h

As energy consumed (E) = P × t

E = 750 × 16

⇒ E = 12000 Wh

⇒ E = 12 kWh

Hence, **electrical energy consumed in 16 hours = 12 kWh**

Question 8

An electrical appliance having a resistance of 200 Ω is operated at 200 V. Calculate the energy consumed by the appliance in 5 minutes (i) in joule, (ii) in kWh

Answer

(i) Given,

Resistance (R) = 200 Ω

Voltage (V) = 200 volt

Time (t) = 5 min = 300 sec

As we know,

$$\text{Energy (E)} = \frac{V^2 t}{R}$$

Substituting the values in the formula above we get,

$$E = \frac{200^2 \times 300}{200}$$

$$\Rightarrow E = 60,000 \text{ J}$$

Hence, **energy consumed = 60,000 J**

(ii) In kWh = ?

As we know,

$$1 \text{ kWh} = 3.6 \times 10^6 \text{ J}$$

$$1 \text{ J} = \frac{1}{3.6 \times 10^6} \text{ kWh}$$

$$60,000 \text{ J} = \frac{60,000}{3.6 \times 10^6}$$

$$\Rightarrow 60,000 \text{ J} = 0.0167 \text{ kWh}$$

Hence, **energy consumed = 0.0167 kWh**

Question 9

A bulb rated 12 V, 24 W operates on a 12 volt battery for 20 minutes. Calculate —

(i) the current flowing through it, and

(ii) the energy consumed.

Answer

(i) Given,

Voltage (V) = 12 V

Power (P) = 24 W

Current (I) = ?

From relation,

Power (P) = VI

Substituting the values in the formula above, we get,

$$24 = 12 \times I$$

$$\Rightarrow I = \frac{24}{12}$$

$$\Rightarrow I = 2 \text{ A}$$

Hence, **the current flowing through it = 2 A**

(ii) Energy (E) = P × t

Time (t) = 20 min = 1200 sec

$E = 24 \times 1200 = 28,800 \text{ J}$

Hence, **energy consumed = 28,800 J**

Question 10

A current of 0.2 A flows through a wire whose ends are at a potential difference of 20 V. Calculate —

(i) the resistance of the wire, and

(ii) the heat energy produced in 1 minute.

Answer

(i) Given,

Current (I) = 0.2 A

Potential difference (V) = 20 V

From Ohm's law

$V = IR$

Substituting the values in the formula above, we get,

$20 = 0.2 \times R$

$\Rightarrow R = \frac{20}{0.2}$

$\Rightarrow R = \frac{200}{2}$

$\Rightarrow R = 100 \Omega$

Hence, **the resistance of the wire = 100 Ω**

(ii) Given,

Time (t) = 60 sec

heat energy produced in 1 minute = ?

From relation,

Heat energy (H) = $I^2 R t$

Substituting the values in the formula above, we get,

$H = 0.2^2 \times 100 \times 60 = 240 \text{ J}$

Question 11

What is the resistance, under normal working conditions, of an electric lamp rated at '240 V, 60 W'? If two such lamps are connected in series across a 240 V mains supply, explain why each one appears less bright.

Answer

Given,

Voltage (V) = 240 V

Power (P) = 60 W

Resistance (R) = ?

From relation

$$P = \frac{V^2}{R}$$

We get,

$$60 = \frac{240^2}{R} \Rightarrow R = \frac{240^2}{60} \Rightarrow R = 960 \Omega$$

Hence, **resistance of the electric lamp = 960 Ω**

From the relation for current through the element, we know,

$$I = \frac{P}{V}$$

Substituting the values in the formula above, we get,

$$I = \frac{60}{240} \Rightarrow I = 0.25 \text{ A}$$

When one lamp is connected across the mains, it draws 0.25 A current. If two such lamps are connected in series across the mains, current through each bulb becomes —

$$\frac{240V}{(960 + 960)\Omega} = 0.125A$$

i.e., current is halved. Hence, heating ($= I^2Rt$) in each bulb becomes one fourth, so each bulb appears less bright.

Question 12

Two bulbs are rated '60 W, 220 V' and '60 W, 110 V' respectively. Calculate the ratio of their resistances.

Answer

Given,

Voltage (V_1) = 220 V

Voltage (V_2) = 110 V

$P = 60$ W (both bulbs have same power)

Resistance (R) = ?

From relation

$$P = \frac{V^2}{R}$$

Case 1:

$$60 = \frac{220^2}{R} \Rightarrow R_1 = \frac{220^2}{60}$$

Case 2:

$$60 = \frac{110^2}{R} \Rightarrow R_2 = \frac{110^2}{60}$$

Ratio between the two is —

$$R_1 : R_2 = \frac{220^2}{60} : \frac{110^2}{60} \quad R_1 : R_2 = \frac{220^2}{110^2} \quad R_1 : R_2 = \frac{220^2}{\frac{110^2}{60}} \quad R_1 : R_2 = \frac{220^2}{110^2} \quad R_1 : R_2 = \frac{2^2}{1^2} \quad R_1 : R_2 = \frac{4}{1}$$

Hence, **ratio of resistances of the two bulbs is = 4 : 1**

Question 13

An electric bulb is rated '250 W, 230 V'. Calculate

(i) the energy consumed in one hour, and

(ii) the time in which the bulb will consume 1.0 kWh energy when connected to 230 V mains?

Answer

(i) Given,

Power (P) = 250 W

Voltage (V) = 230 V

Time (t) = 1 h = 3600 sec

Energy (E) = ?

From relation,

$$E = P \times t$$

Substituting the values in the formula above, we get,

$$E = 250 \times 3600 = 9 \times 10^5 \text{ J}$$

Hence, **energy consumed in one hour = 9×10^5 J**

(ii) Let t be the time in which the bulb will consume 1.0 kWh energy when connected to 230 V mains

$$P = 1.0 \text{ kWh} = 1000 \text{ Wh}$$

Substituting the value in the formula, we get,

$$1000 = 250 \times t$$

$$\Rightarrow t = 1000 / 250 = 4 \text{ h}$$

Hence, **time = 4 h**

Question 14

Three heaters each rated 250 W, 100 V are connected in parallel to a 100 V supply.

Calculate —

- (i) The total current taken from the supply,
- (ii) the resistance of each heater, and
- (iii) the energy supplied in kWh to the three heaters in 5 hours.

Answer

(i) Given,

$$\text{Power (P)} = 250 \text{ W}$$

$$\text{Voltage (V)} = 100 \text{ V}$$

$$\text{Current through each heater (I)} = ?$$

$$\text{As } P = VI$$

Substituting the values in the formula above we get,

$$250 = 100 \times I$$

$$\Rightarrow I = 250 / 100 = 2.5 \text{ A}$$

Hence, **current through each heater = 2.5 A**

Therefore, current for three heaters =

$$I = 3 \times 2.5 = 7.5 \text{ A}$$

Hence, **total current taken from supply = 7.5 A**

(ii) Resistance for each heater (R) = ?

$$\text{Since, } V = IR$$

Substituting the values in the formula above we get,

$$100 = 2.5 \times R$$

$$\Rightarrow R = 100 / 2.5 = 40 \Omega$$

Hence, **resistance of each heater = 40 Ω**

(iii) Energy supplied to three heater in 5 h = ?

$$\text{Energy (E)} = P \times t$$

Substituting the values in the formula above, we get,

$$E = 250 \times 5 = 1250 \text{ Wh} = 1.25 \text{ kWh}$$

$$\text{Hence, Energy for three heaters} = 3 \times 1.25 = 3.75 \text{ kWh}$$

Hence, **energy supplied to the three heaters = 3.75 kWh**

Question 15

A bulb is connected to a battery of p.d. 4 V and internal resistance 2.5 ohm. A steady current of 0.5 A flows through the circuit. Calculate —

- (i) the total energy supplied by the battery in 10 minutes,
- (ii) the resistance of the bulb, and
- (iii) the energy dissipated in the bulb in 10 minutes.

Answer

(i) Given,

$$\text{Voltage (V)} = 4 \text{ V}$$

$$\text{Internal resistance} = 2.5 \Omega$$

$$\text{Current (I)} = 0.5 \text{ A}$$

$$\text{time (t)} = 10 \text{ min} = 600 \text{ sec}$$

$$\text{Energy supplied by the battery (E)} = V \times I \times t$$

Substituting the values in the formula, we get,

$$E = 4 \times 0.5 \times 600 = 1200 \text{ J}$$

Hence, **total energy supplied = 1200 J**

(ii) resistance of the bulb = ?

$$\text{From relation } V = I(R + r)$$

We get,

$$4 = 0.5(R + 2.5)$$

$$\Rightarrow 4 = (0.5 R) + (0.5 \times 2.5)$$

$$\Rightarrow 4 = (0.5 R) + 1.25$$

$$\Rightarrow 0.5 R = 4 - 1.25$$

$$\Rightarrow R = 2.75 / 0.5 = 5.5 \Omega$$

Hence, **resistance of the bulb = 5.5 Ω**

(iii) Energy dissipated in the bulb in 10 min = ?

From relation

$$E = I^2 R t$$

Substituting the values in the formula above, we get,

$$E = 0.5 \times 0.5 \times 5.5 \times 600 = 825 \text{ J}$$

Hence, **energy dissipated = 825 J**

Question 16

Two resistors A and B of resistance 4 Ω and 6 Ω respectively are connected in parallel. The combination is connected across a 6 volt battery of negligible resistance. Calculate : (i) the power supplied by the battery, (ii) the power dissipated in each resistor.

Answer

(i) Given,

Resistance, $R_A = 4 \Omega$

Resistance, $R_B = 6 \Omega$

Let equivalent resistance of the two resistors connected in parallel be R_p

$$\frac{1}{R_p} = \frac{1}{4} + \frac{1}{6} = \frac{3+2}{12} = \frac{5}{12} \Rightarrow R_p = \frac{12}{5} = 2.4 \Omega$$

Hence, equivalent resistance = 2.4 Ω

From relation

$$P = \frac{V^2}{R}$$

We get,

$$P = \frac{6^2}{2.4} \Rightarrow P = 15 \text{ W}$$

Hence, **power supplied = 15 W**

(ii) Power dissipation across each resistor = ?

From relation, $P = VI$

Current across A (4 Ω) resistor —

$$I_A = 6 / 4 = 1.5 \text{ A}$$

Power dissipation across A = VI_A

Substituting we get,

$$P = 6 \times 1.5 = 9 \text{ W}$$

Similarly,

Current across B (6 Ω) resistor —

$$I_B = 6 / 6 = 1 \text{ A}$$

Power dissipation across B resistor = VI_B

Substituting the values in the formula above, we get,

$$P = 6 \times 1 = 6 \text{ W}$$

Hence, **power dissipated across A = 9 W and across B = 6 W**

Question 17

A battery of e.m.f. 15 V and internal resistance 2 Ω is connected to two resistors of resistances 4 Ω and 6 Ω joined in series. Find the electrical energy spent per minute in 6 Ω resistor.

Answer

(i) Given,

e.m.f. (V) = 15 V

Internal resistance = 2 Ω

Resistors are $R_1 = 4 \Omega$ and $R_2 = 6 \Omega$

Electrical energy = ?

As the battery and resistors are connected in series, equivalent resistance is given by

$$R = 2 + 4 + 6 = 12 \Omega$$

From Ohm's law —

$$V = IR$$

Substituting the values in the formula above, we get,

$$15 = I \times 12$$

$$\Rightarrow I = 15 / 12 = 1.25 \text{ A}$$

Hence, **current in circuit = 1.25 A**

Now,

$$\text{Voltage across } 6 \Omega = IR = 1.25 \times 6 = 7.50 \text{ V}$$

Hence, **Voltage across 6 Ω = 7.5 V**

$$\text{Time (t) = 1 min = 60 sec}$$

$$\text{We know, } E = \frac{V^2 \times t}{R}$$

Substituting the values in the formula above, we get,

$$E = \frac{7.5^2 \times 60}{6}$$

$$\Rightarrow E = 7.5^2 \times 10$$

$$\Rightarrow E = 562.5 \text{ J}$$

Hence, **energy spent across the 6 Ω resistor = 562.5 J**

Question 18

Water in an electric kettle connected to a 220 V supply takes 5 minutes to reach its boiling point. How long will it take if the supply voltage falls to 200 V?

Answer

Given,

$$V = 220 \text{ V}$$

$$\text{time (t) = 5 min = 300 sec}$$

From relation

$$P = \frac{V^2}{R}$$

and

Heat produced (H) —

$$H = P \times t$$

$$\Rightarrow H = \frac{V^2}{R} \times t$$

Case 1 for $V = 220 \text{ V}$

$$H = \left(\frac{220^2}{R} \right) \times 300$$

[Equation 1]

Case 2 for $V = 200 \text{ V}$

$$H = \left(\frac{200^2}{R} \right) \times t$$

[Equation 2]

Equating 1 and 2 we get,

$$\left(\frac{220^2}{R} \right) \times 300 = \left(\frac{200^2}{R} \right) \times t \Rightarrow t = \left(\frac{220^2}{200^2} \right) \times 300$$

$$\Rightarrow t = 363 \text{ sec} = 6.05 \text{ min}$$

Hence, **time taken = 6.05 min**

Question 19

An electric toaster draws current 8 A in a circuit with source of voltage 220 V. It is used for 2 h. Find the cost of operating the toaster if the cost of electrical energy is ₹4.50 per kWh.

Answer

Given,

$$I = 8 \text{ A}$$

$$V = 220 \text{ V}$$

$$t = 2 \text{ h}$$

$$\text{rate} = 4.50 \text{ per kWh}$$

$$\text{Cost} = ?$$

From relation,

$$E = V \times I \times t$$

we get,

$$E = 220 \times 8 \times 2 = 3520 \text{ Wh} = 3.52 \text{ kWh}$$

$$\text{As cost of energy for 1 kWh} = ₹ 4.50$$

$$\text{Therefore, cost of energy for 3.52 kWh} = 4.5 \times 3.52$$

$$= ₹15.84$$

$$\text{Hence, cost of electrical energy} = ₹15.84$$

Question 20

An electric iron is rated 220 V, 2 kW. If the iron is used for 3h daily, find the cost of running it for 1 week if it costs ₹ 4.25 per kWh.

Answer

Given,

$$\text{Power (P)} = 2 \text{ kW}$$

$$\text{Voltage (V)} = 220 \text{ V}$$

$$\text{Time (t)} = 7 \times 3 = 21 \text{ h}$$

From relation,

$$E = P \times t$$

Substituting the values in the formula above, we get,

$$E = 2 \times 21 = 42 \text{ kWh}$$

$$\text{cost for 1 kWh of energy} = ₹ 4.25$$

$$\therefore \text{Cost for 42 kWh of energy} = 4.25 \times 42$$

$$= ₹178.50$$

Question 21

A geyser is rated '1500 W, 250 V'. This geyser is connected to 250 V mains. Calculate —

(i) the current drawn,

(ii) the energy consumed in 50 hours, and

(iii) the cost of energy consumed at ₹ 4.20 per kWh.

Answer

(i) Given,

$$P = 1500 \text{ W}$$

$$V = 250 \text{ volt}$$

$$\text{Current drawn (I)} = \frac{P}{V}$$

Substituting the values in the formula, we get,

$$I = \frac{1500}{250}$$

$$\Rightarrow I = 6 \text{ A}$$

$$\text{Hence, current drawn} = 6 \text{ A}$$

(ii) energy consumed in 50 hours = ?

$$t = 50 \text{ h}$$

From relation,

$$E = P \times t$$

Substituting the values in the formula above, we get,

$$E = 1500 \times 50 = 75000 \text{ Wh} = 75 \text{ kWh}$$

Hence, **energy consumed in 50 hours = 75 kWh**

(iii) cost of energy consumed at ₹ 4.20 per kWh = ?

$$\text{Cost per unit of energy} = ₹ 4.20$$

$$\text{Cost for 75 kWh of energy} = 4.2 \times 75$$

$$= ₹ 315$$

Hence, **cost of energy consumed = ₹ 315**